

Lecture Supplement 13

***P28.14** When S is open, R_1 , R_2 , R_3 are in series with the battery. Thus:

$$R_1 + R_2 + R_3 = \frac{6 \text{ V}}{10^{-3} \text{ A}} = 6 \text{ k}\Omega. \quad (1)$$

When S is closed in position 1, the parallel combination of the two R_2 's is in series with R_1 , R_3 , and the battery. Thus:

$$R_1 + \frac{1}{2}R_2 + R_3 = \frac{6 \text{ V}}{1.2 \times 10^{-3} \text{ A}} = 5 \text{ k}\Omega. \quad (2)$$

When S is closed in position 2, R_1 and R_2 are in series with the battery. R_3 is shorted. Thus:

$$R_1 + R_2 = \frac{6 \text{ V}}{2 \times 10^{-3} \text{ A}} = 3 \text{ k}\Omega. \quad (3)$$

From (1) and (3): $R_3 = 3 \text{ k}\Omega$.

Subtract (2) from (1): $R_2 = 2 \text{ k}\Omega$.

From (3): $R_1 = 1 \text{ k}\Omega$.

Answers: $R_1 = 1.00 \text{ k}\Omega, R_2 = 2.00 \text{ k}\Omega, R_3 = 3.00 \text{ k}\Omega$.

P28.20 $+15.0 - (7.00) I_1 - (2.00)(5.00) = 0$

$5.00 = 7.00 I_1$ so $I_1 = 0.714 \text{ A}$

$I_3 = I_1 + I_2 = 2.00 \text{ A}$

$0.714 + I_2 = 2.00$ so $I_2 = 1.29 \text{ A}$

$+\varepsilon - 2.00(1.29) - 5.00(2.00) = 0$ $\varepsilon = 12.6 \text{ V}$

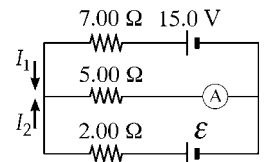


FIG. P28.20

P28.71 (a) After steady-state conditions have been reached, there is no DC current through the capacitor.

Thus, for R_3 : $I_{R_3} = 0$ (steady-state).

For the other two resistors, the steady-state current is simply determined by the 9.00-V emf across the 12-k Ω and 15-k Ω resistors in series:

For R_1 and R_2 :

$$I_{(R_1+R_2)} = \frac{\varepsilon}{R_1 + R_2} = \frac{9.00 \text{ V}}{(12.0 \text{ k}\Omega + 15.0 \text{ k}\Omega)} = 333 \mu\text{A} \text{ (steady-state)}$$

- (b) After the transient currents have ceased, the potential difference across C is the same as the potential difference across $R_2 (= R_2)$ because there is no voltage drop across R_3 . Therefore, the charge Q on C is

$$Q = C(\Delta V)_{R_2} = C(I R_2) = (10.0 \mu\text{F})(333 \mu\text{A})(15.0 \text{k}\Omega) = \boxed{50.0 \mu\text{C}} .$$

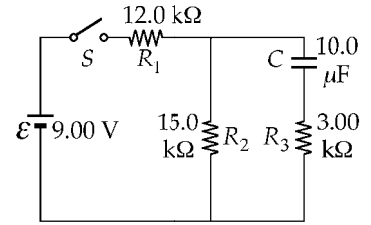


FIG. P28.71(b)

- (c) When the switch is opened, the branch containing R_1 is no longer part of the circuit. The capacitor discharges through $(R_2 + R_3)$ with a time constant of $(R_2 + R_3)C = (15.0 \text{k}\Omega + 3.00 \text{k}\Omega)(10.0 \mu\text{F}) = 0.180 \text{s}$. The initial current I_i in this discharge circuit is determined by the initial potential difference across the capacitor applied to $(R_2 + R_3)$ in series:

$$I_i = \frac{(\Delta V)_C}{(R_2 + R_3)} = \frac{I R_2}{(R_2 + R_3)} = \frac{(333 \mu\text{A})(15.0 \text{k}\Omega)}{(15.0 \text{k}\Omega + 3.00 \text{k}\Omega)} = 278 \mu\text{A} .$$

Thus, when the switch is opened, the current through R_2 changes instantaneously from $333 \mu\text{A}$ (downward) to $278 \mu\text{A}$ (downward) as shown in the graph. Thereafter, it decays according to

$$I_{R_2} = I_i e^{-t/(R_2 + R_3)C} = \boxed{(278 \mu\text{A}) e^{-t/(0.180 \text{s})} \text{ (for } t > 0)} .$$

- (d) The charge q on the capacitor decays from Q_i to $\frac{Q_i}{5}$ according to

$$\begin{aligned} q &= Q_i e^{-t/(R_2 + R_3)C} \\ \frac{Q_i}{5} &= Q_i e^{-t/(0.180 \text{s})} \\ 5 &= e^{t/0.180 \text{s}} \\ \ln 5 &= \frac{t}{180 \text{ m s}} \\ t &= (0.180 \text{s})(\ln 5) = \boxed{290 \text{ m s}} \end{aligned}$$

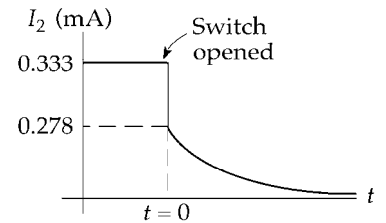


FIG. P28.71(c)

Sign convention for the second rule:

- If a resistor R is traversed in the direction of the current;
 $\Delta V = -IR$. (Current flows from a higher potential to a lower potential)
- If a resistor R is traversed in the direction opposite the current;
 $\Delta V = IR$.
- If a source of emf (assumed to have no internal resistance) is traversed in from $-$ to $+$; $\Delta V = \varepsilon$.
- If a source of emf (assumed to have no internal resistance) is traversed in from $+$ to $-$; $\Delta V = -\varepsilon$.
- if the battery has an internal resistance r , it has to be treated as a regular resistance in series with the battery; $\Delta V = \varepsilon - Ir$.

