

## PHYS 232

### Homework #4 Solutions

25.60 The positive plate by itself creates a field  $E = \frac{\sigma}{2\epsilon_0} = \frac{36.0 \times 10^{-9} \text{ C/m}^2}{2(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)} = 2.03 \frac{\text{kN}}{\text{C}}$

away from the + plate. The negative plate by itself creates the same size field and between the plates it is in the same direction. Together the plates create a uniform field 4.07 kN/C in the space between.

- (a) Take  $V = 0$  at the negative plate. The potential at the positive plate is then

$$V - 0 = -\int_0^{12.0 \text{ cm}} (-4.07 \text{ kN/C}) dx$$

The potential difference between the plates is  $V = (4.07 \times 10^3 \text{ N/C})(0.120 \text{ m}) = \boxed{488 \text{ V}}$

(b)  $\left(\frac{1}{2}mv^2 + qV\right)_i = \left(\frac{1}{2}mv_f^2 + qV\right)_f$

$$qV = (1.60 \times 10^{-19} \text{ C})(488 \text{ V}) = \frac{1}{2}mv_f^2 = \boxed{7.81 \times 10^{-17} \text{ J}}$$

(c)  $v_f = \boxed{306 \text{ km/s}}$

26.4 (a)  $C = 4\pi\epsilon_0 R$

$$R = \frac{C}{4\pi\epsilon_0} = k_e C = (8.99 \times 10^9 \text{ N} \cdot \text{m}^2/\text{C}^2)(1.00 \times 10^{-12} \text{ F}) = \boxed{8.99 \text{ mm}}$$

(b)  $C = 4\pi\epsilon_0 R = \frac{4\pi(8.85 \times 10^{-12} \text{ C}^2)(2.00 \times 10^{-3} \text{ m})}{\text{N} \cdot \text{m}^2} = \boxed{0.222 \text{ pF}}$

(c)  $Q = CV = (2.22 \times 10^{-13} \text{ F})(100 \text{ V}) = \boxed{2.22 \times 10^{-11} \text{ C}}$


26.8  $C = \frac{\kappa\epsilon_0 A}{d} = 60.0 \times 10^{-15} \text{ F}$

$$d = \frac{\kappa\epsilon_0 A}{C} = \frac{(1)(8.85 \times 10^{-12})(21.0 \times 10^{-12})}{60.0 \times 10^{-15}}$$

$$d = 3.10 \times 10^{-9} \text{ m} = \boxed{3.10 \text{ nm}}$$

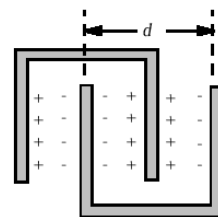26.10 With  $\theta = \pi$ , the plates are out of mesh and the overlap area is zero. With  $\theta = 0$ , the overlap area is that of a semi-circle,  $\pi R^2/2$ . By proportion, the effective area of a single sheet of charge is  $(\pi - \theta)R^2/2$ .


When there are two plates in each comb, the number of adjoining sheets of positive and negative charge is 3, as shown in the sketch. When there are  $N$  plates on each comb, the number of parallel capacitors is  $2N - 1$  and the total capacitance is



$$C = (2N - 1) \frac{\epsilon_0 A_{\text{effective}}}{\text{distance}} = \frac{(2N - 1)\epsilon_0 (\pi - \theta)R^2/2}{d/2} = \boxed{\frac{(2N - 1)\epsilon_0 (\pi - \theta)R^2}{d}}$$

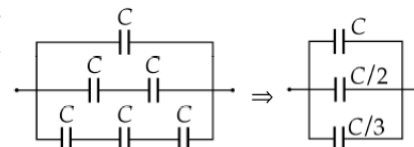26.22 The circuit reduces first according to the rule for capacitors in series, as shown in the figure, then according to the rule for capacitors in parallel, shown below.

$$C_{\text{eq}} = C \left( 1 + \frac{1}{2} + \frac{1}{3} \right) = \frac{11}{6} C = \boxed{1.83C}$$



26.23  $C = \frac{Q}{\Delta V}$  so  $6.00 \times 10^{-6} = \frac{Q}{20.0}$  and  $Q = \boxed{120 \mu\text{C}}$


$Q_1 = 120 \mu\text{C} - Q_2$  and  $\Delta V = \frac{Q}{C}$

$\frac{120 - Q_2}{C_1} = \frac{Q_2}{C_2}$  or  $\frac{120 - Q_2}{6.00} = \frac{Q_2}{3.00}$

$(3.00)(120 - Q_2) = (6.00)Q_2$

$Q_2 = \frac{360}{9.00} = \boxed{40.0 \mu\text{C}}$

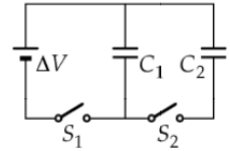$Q_1 = 120 \mu\text{C} - 40.0 \mu\text{C} = \boxed{80.0 \mu\text{C}}$



\*26.45 (a) With air between the plates, we find  $C_0 = \frac{Q}{\Delta V} = \frac{48.0 \mu\text{C}}{12.0 \text{ V}} = \boxed{4.00 \mu\text{F}}$

- (b) When Teflon is inserted, the charge remains the same ( $48.0 \mu\text{C}$ ) because the plates are isolated. However, the capacitance, and hence the voltage, changes. The new capacitance is

$C' = \kappa C_0 = 2.10(4.00 \mu\text{F}) = \boxed{8.40 \mu\text{F}}$

(c) The voltage on the capacitor now is  $\Delta V' = \frac{Q}{C'} = \frac{48.0 \mu\text{C}}{8.40 \mu\text{F}} = \boxed{5.71 \text{ V}}$

and the charge is  $\boxed{48.0 \mu\text{C}}$

26.47  $\frac{1}{C} = \frac{1}{\left(\frac{\kappa_1 ab}{k_e(b-a)}\right)} + \frac{1}{\left(\frac{\kappa_2 bc}{k_e(c-b)}\right)} = \frac{k_e(b-a)}{\kappa_1 ab} + \frac{k_e(c-b)}{\kappa_2 bc}$


$C = \frac{1}{\frac{k_e(b-a)}{\kappa_1 ab} + \frac{k_e(c-b)}{\kappa_2 bc}} = \frac{\kappa_1 \kappa_2 abc}{k_e \kappa_2 (bc - ac) + k_e \kappa_1 (ac - ab)} = \boxed{\frac{4\pi \kappa_1 \kappa_2 abc \epsilon_0}{\kappa_2 bc - \kappa_1 ab + (\kappa_1 - \kappa_2) ac}}$

26.54 (a)  $C = \left[ \frac{1}{3.00} + \frac{1}{6.00} \right]^{-1} + \left[ \frac{1}{2.00} + \frac{1}{4.00} \right]^{-1} = \boxed{3.33 \mu\text{F}}$

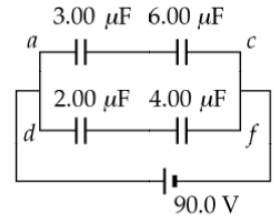(c)  $Q_{ac} = C_{ac} (\Delta V_{ac}) = (2.00 \mu\text{F})(90.0 \text{ V}) = 180 \mu\text{C}$

Therefore,  $Q_3 = Q_6 = \boxed{180 \mu\text{C}}$

$Q_{df} = C_{df} (\Delta V_{df}) = (1.33 \mu\text{F})(90.0 \text{ V}) = \boxed{120 \mu\text{C}}$



(b)  $\Delta V_3 = \frac{Q_3}{C_3} = \frac{180 \mu\text{C}}{3.00 \mu\text{F}} = \boxed{60.0 \text{ V}}$

$\Delta V_6 = \frac{Q_6}{C_6} = \frac{180 \mu\text{C}}{6.00 \mu\text{F}} = \boxed{30.0 \text{ V}}$

$\Delta V_2 = \frac{Q_2}{C_2} = \frac{120 \mu\text{C}}{2.00 \mu\text{F}} = \boxed{60.0 \text{ V}}$

$\Delta V_4 = \frac{Q_4}{C_4} = \frac{120 \mu\text{C}}{4.00 \mu\text{F}} = \boxed{30.0 \text{ V}}$

(d)  $U_T = \frac{1}{2} C_{\text{eq}} (\Delta V)^2 = \frac{1}{2} (3.33 \times 10^{-6})(90.0 \text{ V})^2 = \boxed{13.4 \text{ mJ}}$

26.61 Note that the potential difference between the plates is held constant at  $\Delta V_i$  by the battery.

$$C_i = \frac{q_0}{\Delta V_i} \quad \text{and} \quad C_f = \frac{q_f}{\Delta V_i} = \frac{q_0 + q}{\Delta V_i}$$

But  $C_f = \kappa C_i$ , so  $\frac{q_0 + q}{\Delta V_i} = \kappa \left( \frac{q_0}{\Delta V_i} \right)$

Thus,  $\kappa = \frac{q_0 + q}{q_0}$  or  $\kappa = \boxed{1 + \frac{q}{q_0}}$

## Homework #5 Solutions

27.9 (a)  $J = \frac{I}{A} = \frac{5.00 \text{ A}}{\pi(4.00 \times 10^{-3} \text{ m})^2} = \boxed{99.5 \text{ kA/m}^2}$

(b)  $J_2 = \frac{1}{4} J_1; \quad \frac{I}{A_2} = \frac{1}{4} \frac{I}{A_1}$

$$A_1 = \frac{1}{4} A_2 \quad \text{so} \quad \pi(4.00 \times 10^{-3})^2 = \frac{1}{4} \pi r_2^2$$

$$r_2 = 2(4.00 \times 10^{-3}) = 8.00 \times 10^{-3} \text{ m} = \boxed{8.00 \text{ mm}}$$

27.14 (a) Applying its definition, we find the resistance of the rod,

$$R = \frac{\Delta V}{I} = \frac{15.0 \text{ V}}{4.00 \times 10^{-3} \text{ A}} = 3750 \Omega = \boxed{3.75 \text{ k}\Omega}$$

(b) The length of the rod is determined from Equation 27.11:  $R = \rho \ell / A$ . Solving for  $\ell$  and substituting numerical values for  $R$ ,  $A$ , and the values of  $\rho$  given for carbon in Table 27.1, we obtain

$$\ell = \frac{RA}{\rho} = \frac{(3.75 \times 10^3 \Omega)(5.00 \times 10^{-6} \text{ m}^2)}{(3.50 \times 10^{-5} \Omega \cdot \text{m})} = \boxed{536 \text{ m}}$$

27.24  $R = \frac{\rho_1 l_1}{A_1} + \frac{\rho_2 l_2}{A_2} = (\rho_1 l_1 + \rho_2 l_2) / d^2$

$$R = \frac{(4.00 \times 10^{-3} \Omega \cdot \text{m})(0.250 \text{ m}) + (6.00 \times 10^{-3} \Omega \cdot \text{m})(0.400 \text{ m})}{(3.00 \times 10^{-3} \text{ m})^2} = \boxed{378 \Omega}$$

27.49 At operating temperature,

(a)  $P = I(\Delta V) = (1.53 \text{ A})(120 \text{ V}) = \boxed{184 \text{ W}}$

(b) Use the change in resistance to find the final operating temperature of the toaster.

$$R = R_0(1 + \alpha \Delta T)$$

$$\frac{120}{1.53} = \frac{120}{1.80} [1 + (0.400 \times 10^{-3})\Delta T]$$

$$\Delta T = 441^\circ\text{C}$$

$$T = 20.0^\circ\text{C} + 441^\circ\text{C} = \boxed{461^\circ\text{C}}$$

\*27.52 (a)  $I = \frac{\Delta V}{R}$  so  $P = (\Delta V)I = \frac{(\Delta V)^2}{R}$

$$R = \frac{(\Delta V)^2}{\mathcal{P}} = \frac{(120 \text{ V})^2}{25.0 \text{ W}} = \boxed{576 \Omega}$$

and  $R = \frac{(\Delta V)^2}{\mathcal{P}} = \frac{(120 \text{ V})^2}{100 \text{ W}} = \boxed{144 \Omega}$

(b)  $I = \frac{\mathcal{P}}{\Delta V} = \frac{25.0 \text{ W}}{120 \text{ V}} = 0.208 \text{ A} = \frac{Q}{t} = \frac{1.00 \text{ C}}{t}$

$$t = \frac{1.00 \text{ C}}{0.208 \text{ A}} = \boxed{4.80 \text{ s}}$$

The charge has **lower potential energy**.

(c)  $P = 25.0 \text{ W} = \frac{\Delta U}{t} = \frac{1.00 \text{ J}}{t}$

$$t = \frac{1.00 \text{ J}}{25.0 \text{ W}} = \boxed{0.0400 \text{ s}}$$

The energy **changes from electrical to heat and light**.

(d)  $\Delta U = P t = (25.0 \text{ J/s})(86400 \text{ s/d})(30.0 \text{ d}) = 64.8 \times 10^6 \text{ J}$

The energy company sells **energy**.

$$\text{Cost} = 64.8 \times 10^6 \text{ J} \left( \frac{\$0.0700}{\text{kWh}} \right) \left( \frac{\text{k}}{1000} \right) \left( \frac{\text{W} \cdot \text{s}}{\text{J}} \right) \left( \frac{\text{h}}{3600 \text{ s}} \right) = \boxed{\$1.26}$$

$$\text{Cost per joule} = \frac{\$0.0700}{\text{kWh}} \left( \frac{\text{kWh}}{3.60 \times 10^6 \text{ J}} \right) = \boxed{\$1.94 \times 10^{-8} / \text{J}}$$

27.66 (a)  $R = \frac{\rho l}{A} = \frac{\rho L}{\pi(r_b^2 - r_a^2)}$

(b)  $R = \frac{(3.50 \times 10^5 \Omega \cdot \text{m})(0.0400 \text{ m})}{\pi[(0.0120 \text{ m})^2 - (0.00500 \text{ m})^2]} = 3.74 \times 10^7 \Omega = \boxed{37.4 \text{ M}\Omega}$


(c)  $dR = \frac{\rho dl}{A} = \frac{\rho dr}{(2\pi r)L} = \left(\frac{\rho}{2\pi L}\right) \frac{dr}{r}$ , so  $R = \frac{\rho}{2\pi L} \int_{r_a}^{r_b} \frac{dr}{r} = \frac{\rho}{2\pi L} \ln\left(\frac{r_b}{r_a}\right)$

(d)  $R = \frac{(3.50 \times 10^5 \Omega \cdot \text{m})}{2\pi(0.0400 \text{ m})} \ln\left(\frac{1.20}{0.500}\right) = 1.22 \times 10^6 \Omega = \boxed{1.22 \text{ M}\Omega}$

28.3 The total resistance is  $R = \frac{3.00 \text{ V}}{0.600 \text{ A}} = 5.00 \Omega$


(a)  $R_{\text{lamp}} = R - r_{\text{batteries}} = 5.00 \Omega - 0.408 \Omega = \boxed{4.59 \Omega}$

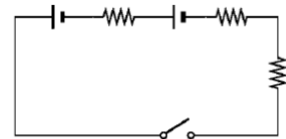(b)  $\frac{P_{\text{batteries}}}{P_{\text{total}}} = \frac{(0.408 \Omega)I^2}{(5.00 \Omega)I^2} = 0.0816 = \boxed{8.16\%}$



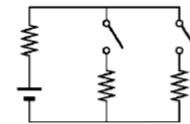28.4 (a) Here  $\mathcal{E} = I(R+r)$ , so  $I = \frac{\mathcal{E}}{R+r} = \frac{12.6 \text{ V}}{(5.00 \Omega + 0.0800 \Omega)} = 2.48 \text{ A}$

Then,  $\Delta V = IR = (2.48 \text{ A})(5.00 \Omega) = \boxed{12.4 \text{ V}}$



(b) Let  $I_1$  and  $I_2$  be the currents flowing through the battery and the headlights, respectively.

Then,  $I_1 = I_2 + 35.0 \text{ A}$ , and  $\mathcal{E} - I_1 r - I_2 R = 0$

so  $\mathcal{E} = (I_2 + 35.0 \text{ A})(0.0800 \Omega) + I_2(5.00 \Omega) = 12.6 \text{ V}$

giving  $I_2 = 1.93 \text{ A}$

Thus,  $\Delta V_2 = (1.93 \text{ A})(5.00 \Omega) = \boxed{9.65 \text{ V}}$

28.15  $R_p = \left( \frac{1}{3.00} + \frac{1}{1.00} \right)^{-1} = 0.750 \Omega$

$$R_s = (2.00 + 0.750 + 4.00) \Omega = 6.75 \Omega$$

$$I_{\text{battery}} = \frac{\Delta V}{R_s} = \frac{18.0 \text{ V}}{6.75 \Omega} = 2.67 \text{ A}$$

$$P = I^2 R: \quad P_2 = (2.67 \text{ A})^2 (2.00 \Omega)$$

$$P_2 = \boxed{14.2 \text{ W}} \text{ in } 2.00 \Omega$$




$$P_4 = (2.67 \text{ A})^2 (4.00 \Omega) = \boxed{28.4 \text{ W}} \text{ in } 4.00 \Omega$$

$$\Delta V_2 = (2.67 \text{ A})(2.00 \Omega) = 5.33 \text{ V}, \quad \Delta V_4 = (2.67 \text{ A})(4.00 \Omega) = 10.67 \text{ V}$$

$$\Delta V_p = 18.0 \text{ V} - \Delta V_2 - \Delta V_4 = 2.00 \text{ V} \quad (= \Delta V_3 = \Delta V_1)$$

$$P_3 = \frac{(\Delta V_3)^2}{R_3} = \frac{(2.00 \text{ V})^2}{3.00 \Omega} = \boxed{1.33 \text{ W}} \text{ in } 3.00 \Omega$$
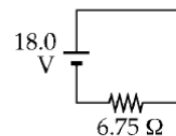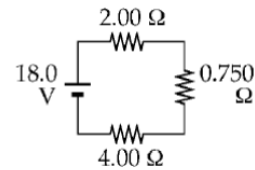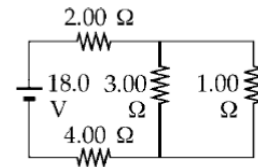
$$P_1 = \frac{(\Delta V_1)^2}{R_1} = \frac{(2.00 \text{ V})^2}{1.00 \Omega} = \boxed{4.00 \text{ W}} \text{ in } 1.00 \Omega$$






28.17 (a)  $\Delta V = IR$ :  $33.0 \text{ V} = I_1(11.0 \ \Omega)$   $33.0 \text{ V} = I_2(22.0 \ \Omega)$

$$I_1 = 3.00 \text{ A} \quad I_2 = 1.50 \text{ A}$$

$$P = I^2 R: \quad P_1 = (3.00 \text{ A})^2(11.0 \ \Omega) \quad P_2 = (1.50 \text{ A})^2(22.0 \ \Omega)$$

$$P_1 = 99.0 \text{ W} \quad P_2 = 49.5 \text{ W}$$

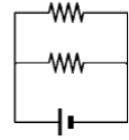

The 11.0- $\Omega$  resistor uses more power.


(b)  $P_1 + P_2 = \boxed{148 \text{ W}}$   $P = I(\Delta V) = (4.50)(33.0) = \boxed{148 \text{ W}}$

(c)  $R_s = R_1 + R_2 = 11.0 \ \Omega + 22.0 \ \Omega = 33.0 \ \Omega$

$$\Delta V = IR: \quad 33.0 \text{ V} = I(33.0 \ \Omega), \text{ so } I = 1.00 \text{ A}$$

$$P = I^2 R: \quad P_1 = (1.00 \text{ A})^2(11.0 \ \Omega) \quad P_2 = (1.00 \text{ A})^2(22.0 \ \Omega)$$

$$P_1 = 11.0 \text{ W} \quad P_2 = 22.0 \text{ W}$$

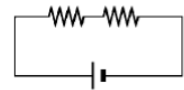

The 22.0- $\Omega$  resistor uses more power.

(d)  $P_1 + P_2 = I^2(R_1 + R_2) = (1.00 \text{ A})^2(33.0 \ \Omega) = \boxed{33.0 \text{ W}}$

$$P = I(\Delta V) = (1.00 \text{ A})(33.0 \text{ V}) = \boxed{33.0 \text{ W}}$$

(e) The parallel configuration uses more power.