

Combination of Capacitors

Parallel combination

- The individual potential differences across capacitors connected in parallel are all the same and are equal to the potential difference applied across the combination.

- For a parallel combination total charge Q ,

$$Q = Q_1 + Q_2 \tag{30}$$

- Because the voltages are the same:

$$Q_1 = C_1 \Delta V \quad Q_2 = C_2 \Delta V \tag{31}$$

- For a capacitor equivalent to the combination;

$$Q = C_{eq} \Delta V \tag{32}$$

- Substituting:

$$C_{eq} \Delta V = C_1 \Delta V + C_2 \Delta V \tag{33}$$


$$C_{eq} = C_1 + C_2 \tag{34}$$

For a parallel combination of many capacitors:


$$C_{eq} = C_1 + C_2 + C_3 + C_4 \dots \tag{35}$$

The equivalent capacitance of a parallel combination of capacitors is greater than any of the individual capacitances.

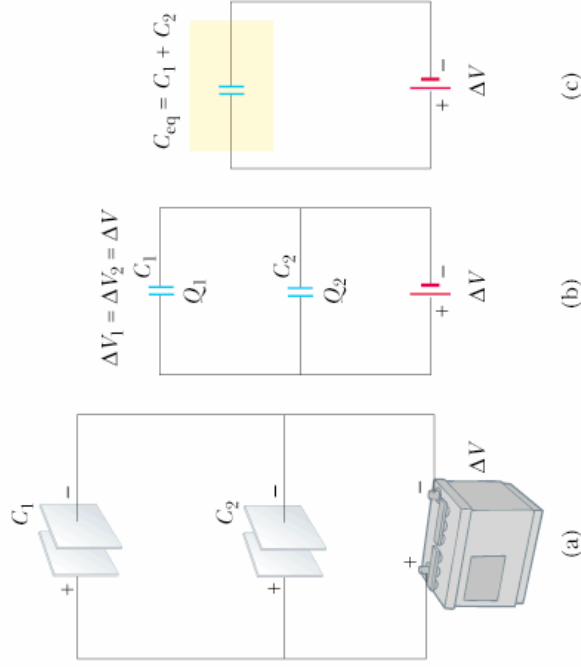
Serway, Physics for Scientists and Engineers, 5/e
Figure 26.8



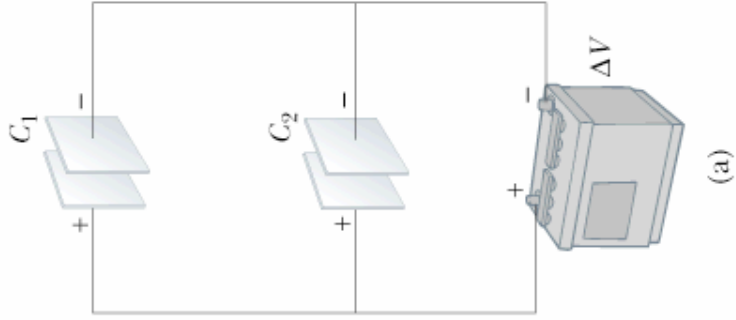Serway, Physics for Scientists and Engineers, 5/e
Figure 26.8



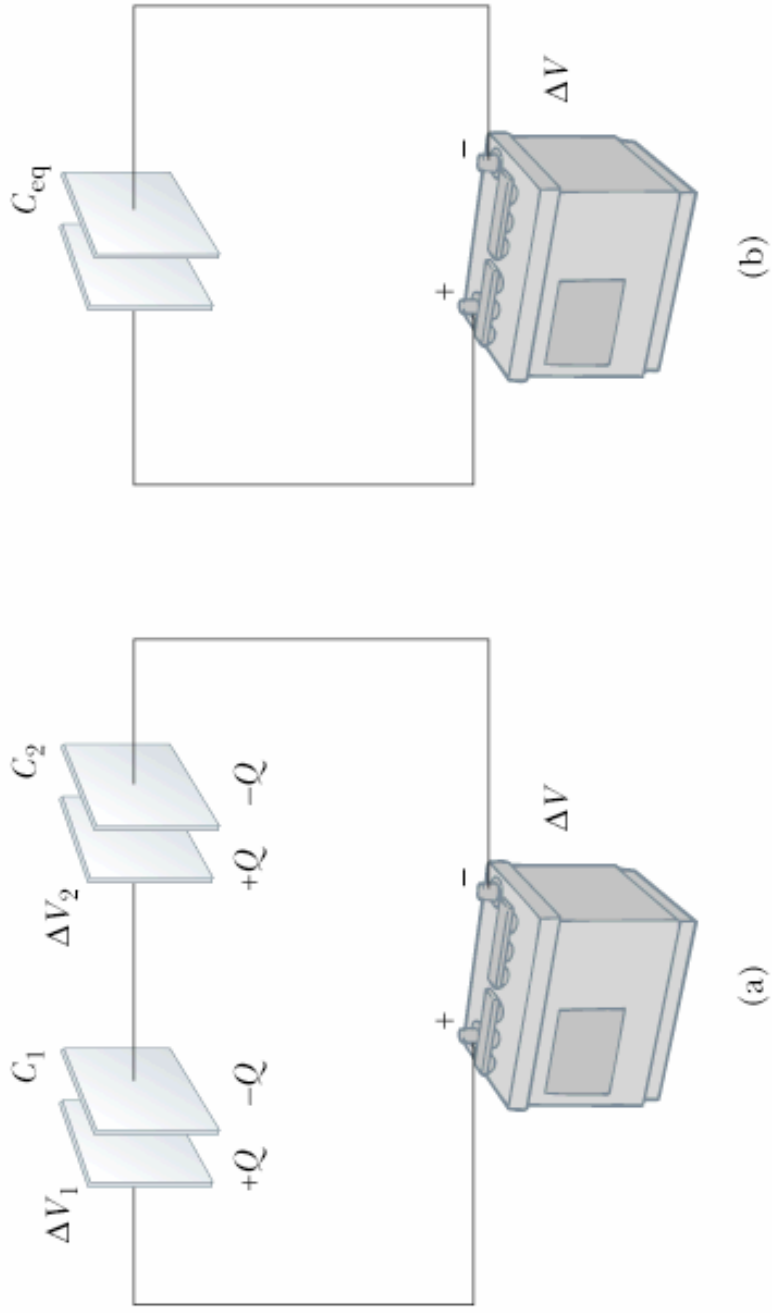Serway, Physics for Scientists and Engineers, 5/e
Figure 26.9



Series combination

- The charges on capacitors connected in series are the same
- For a series combination total voltage ΔV ,

$$\Delta V = \Delta V_1 + \Delta V_2 \quad (36)$$

- Because the charges are the same:

$$\Delta V_1 = \frac{Q}{C_1} \quad \Delta V_2 = \frac{Q}{C_2} \quad (37)$$

- For a capacitor equivalent to the combination;

$$\Delta V = \frac{Q}{C_{eq}} \quad (38)$$

- Substituting:

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2} \quad (39)$$


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \quad (40)$$

- For a series combination of many capacitors:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \dots \quad (41)$$

- The equivalent capacitance of a series combination of capacitors is always less than any individual capacitance in the combination.


Serway, Physics for Scientists and Engineers, 5/e
Figure 26.9

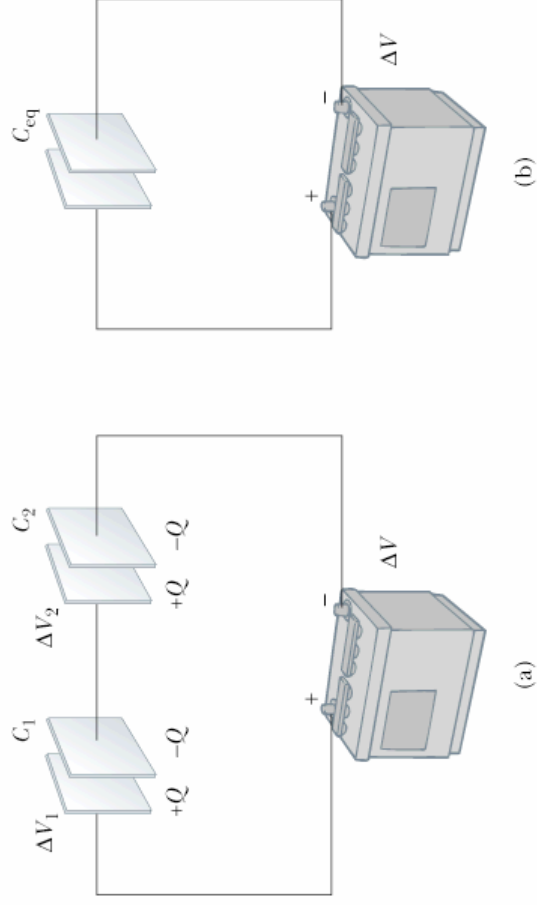

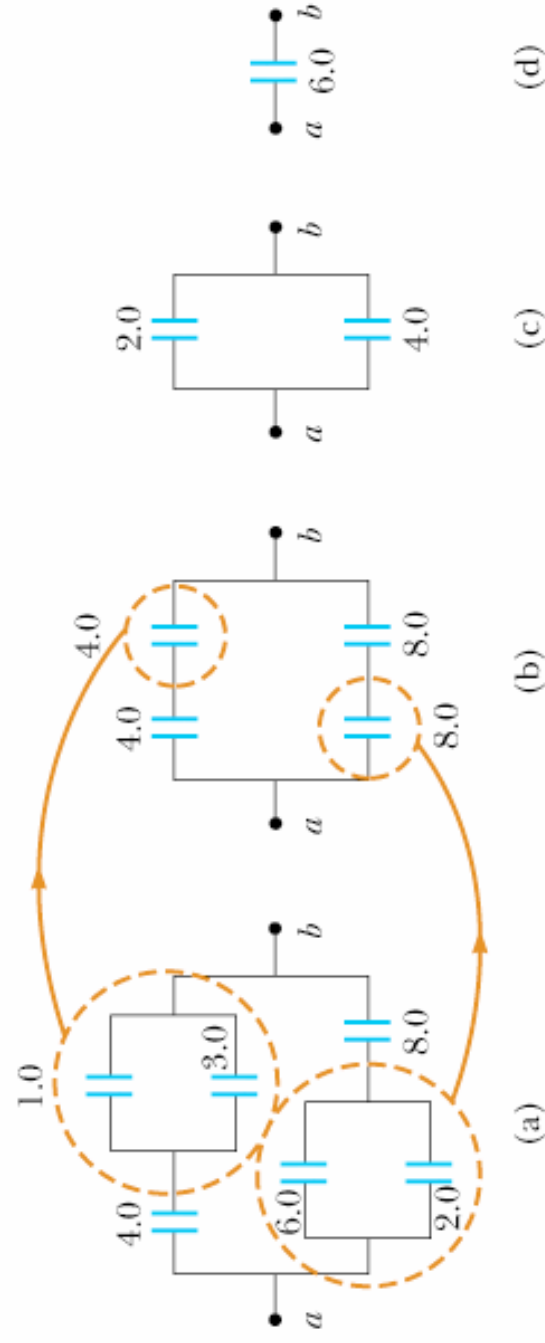Example 26.4

Find the equivalent capacitance between a and b for the combination shown.

Serway, Physics for Scientists and Engineers, 5/e
Figure 26.10



Energy stored in a capacitor

- We have to spend energy to charge the capacitor (energy from the battery), this energy is stored in the electric field of the charged capacitor as potential energy.
- Suppose that we charge the capacitor by moving small amounts of charge dq from one plate the other.
- Assume that at any given time the plates have charges $-q$ and q .
- Potential difference between the plates

$$\Delta V = \frac{q}{C} \quad (42)$$

- Amount of work required to move dq between the plates.

$$dW = dq\Delta V = \frac{q}{C}dq \quad (43)$$

- Amount of work required to charge the capacitor from $q = 0$ to $q = Q$:

$$W = \int_0^Q dW \quad (44)$$

$$= \int_0^Q \frac{q}{C}dq \quad (45)$$

$$= \frac{1}{2C} [q^2]_0^Q \quad (46)$$

$$W = \frac{Q^2}{2C} \quad (47)$$


- Potential energy U stored in the capacitor:

$$U = W = \frac{Q^2}{2C} \quad (48)$$

- Substituting from $C = \frac{Q}{\Delta V}$:

$$U = \frac{Q^2}{2C} = \frac{1}{2}Q\Delta V = \frac{1}{2}C(\Delta V)^2 \quad (49)$$

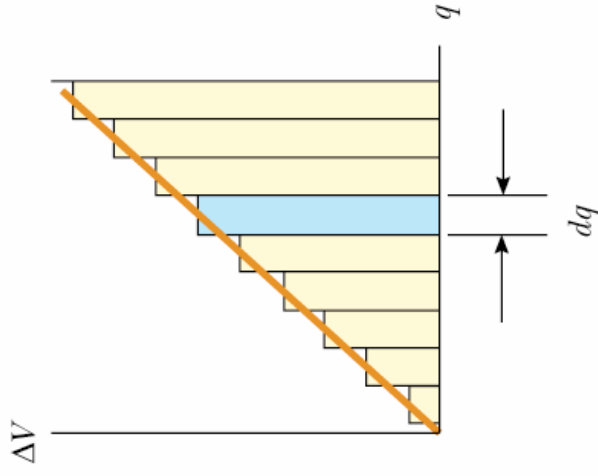Serway, Physics for Scientists and Engineers, 5/e
Figure 26.11



Energy stored in a capacitor

- Energy is stored in the electric field of the charged capacitor. Consider a parallel plate capacitor.
- Using $\Delta V = Ed$, and $C = \frac{\epsilon_0 A}{d}$ (for a parallel plate capacitor)

$$U = \frac{1}{2} \frac{\epsilon_0 A}{d} (Ed)^2 = \frac{1}{2} (\epsilon_0 Ad) E^2 \quad (50)$$


- But Ad is the volume occupied by the electric field. Hence **Energy per unit volume of the electric field** or **energy density** of the electric field is:

$$u_E = \frac{1}{2} (\epsilon_0 Ad) E^2 / Ad \quad (51)$$



$$u_E = \frac{1}{2} \epsilon_0 E^2 \quad (52)$$

- This is a general result: **energy density of the electric field is proportional to the square of the magnitude of the electric field at a given point**

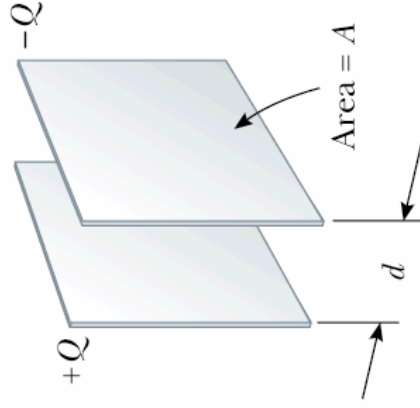
Serway, Physics for Scientists and Engineers, 5/e
Figure 26.2



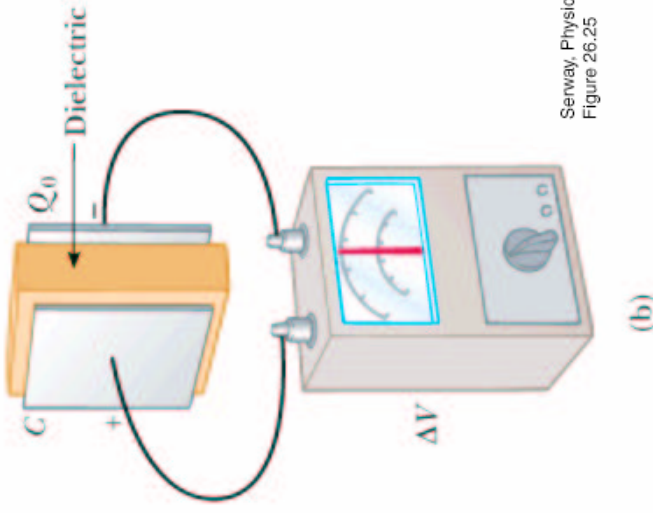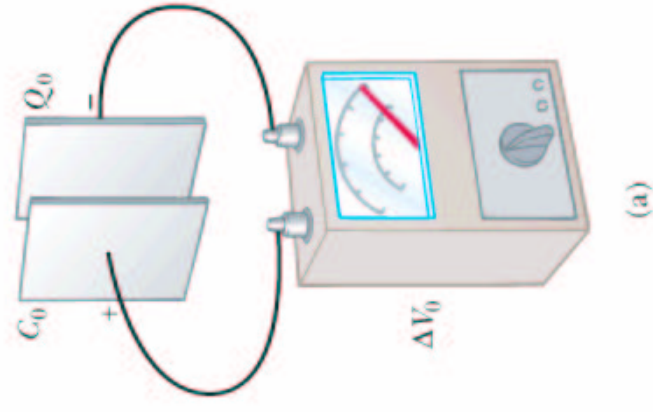Serway, Physics for Scientists and Engineers, 5/e
Figure 26.14



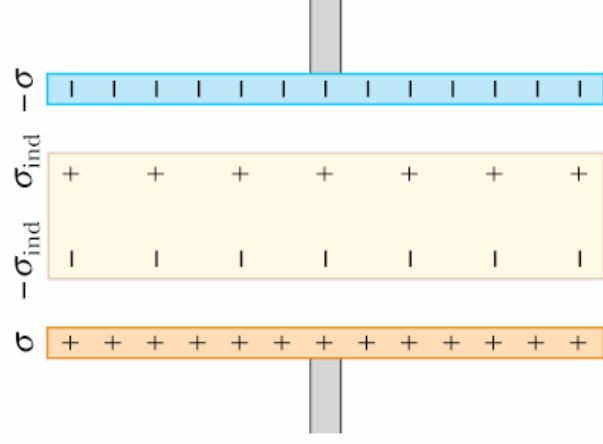Serway, Physics for Scientists and Engineers, 5/e
Figure 26.25



Capacitors with Dielectrics

- A dielectric in a non-conducting material that lowers the electric field, hence the voltage of a capacitor for a given charge Q .

$$\Delta V = \frac{\Delta V_0}{\kappa} \quad (53)$$

- κ is the **dielectric constant** of the material and is larger than 1. ($\kappa = 1$ for vacuum)
- If the capacitance, charge and the voltage of the capacitor without dielectric are C_0 , Q_0 , and ΔV_0 , capacitance C of the capacitor with the dielectric:

$$C = \frac{Q_0}{\Delta V} \quad (54)$$

$$= \frac{Q_0}{\Delta V_0/\kappa} \quad (55)$$

$$= \kappa \frac{Q_0}{\Delta V_0} \quad (56)$$

$$C = \kappa C_0 \quad (57)$$

- **The capacitance increases by factor κ when the dielectric completely fills the region between the plates.**

- For a parallel plate capacitor with a dielectric in:

$$C = \kappa \frac{\epsilon_0 A}{d} \quad (58)$$


- In addition to increasing the capacitance of a capacitor, dielectrics also increase the maximum electric field that can be applied on a capacitor without causing a discharge. This maximum electric field is known as the **dielectric strength**

Example 26.7

A parallel plate capacitor is charged with a battery to a charge Q_0 . Battery is then removed and a slab of material with dielectric constant κ is inserted between the plates. Find the energy stored in the capacitor before and after the dielectric is inserted.

$$U = \frac{Q^2}{2C} \quad (59)$$

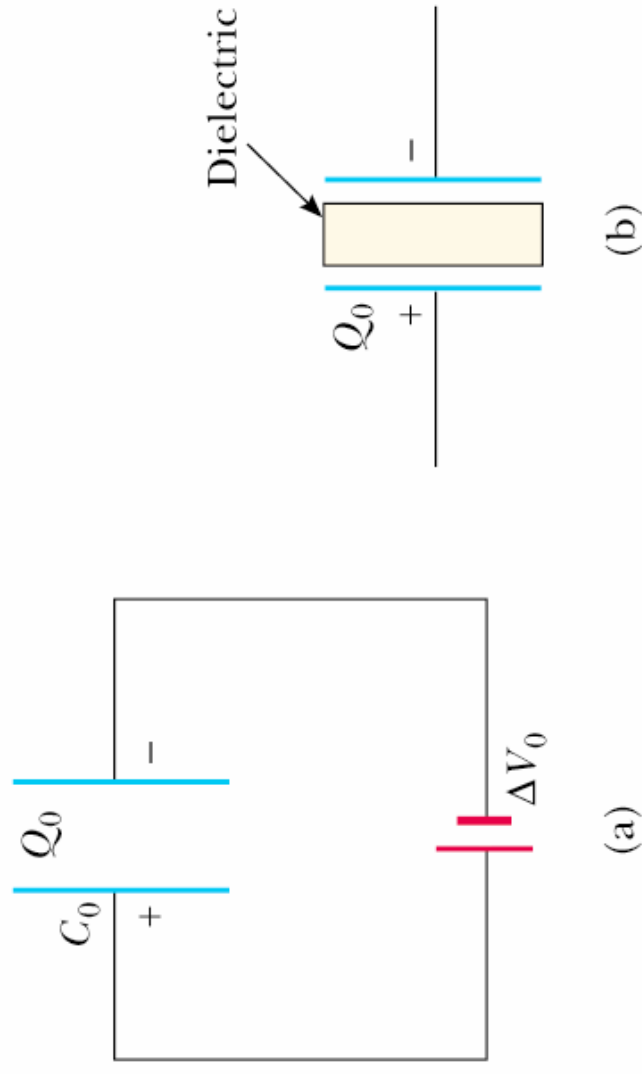Serway, Physics for Scientists and Engineers, 5/e
Figure 26.17



Serway, Physics for Scientists and Engineers, 5/e
Figure 26.15

