

ohm's Law

- We know that:

$$J = \frac{I}{A}$$

and;

$$El = \Delta V$$

-

$$\mathbf{J} = \sigma \mathbf{E}$$


$$\frac{I}{A} = \sigma \frac{\Delta V}{l}$$

$$I = \sigma \frac{A}{l} \Delta V$$


$$I = \frac{A}{l\rho} \Delta V$$

$$I = \frac{\Delta V}{R}$$

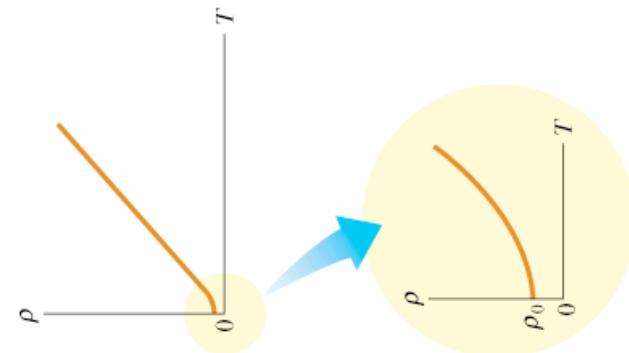
Serway, Physics for Scientists and Engineers, 5/e
Figure 27.10



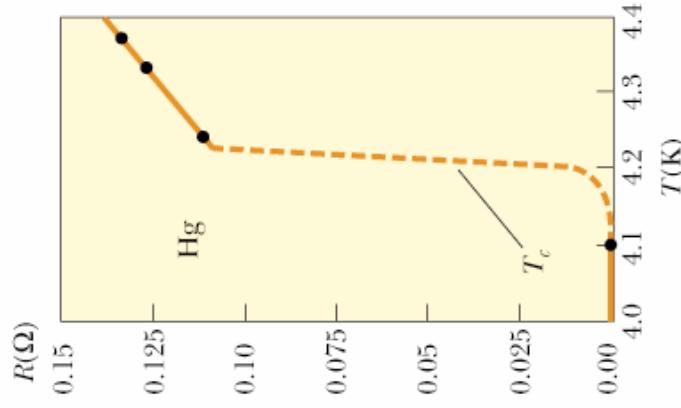Serway, Physics for Scientists and Engineers, 5/e
Figure 27.12



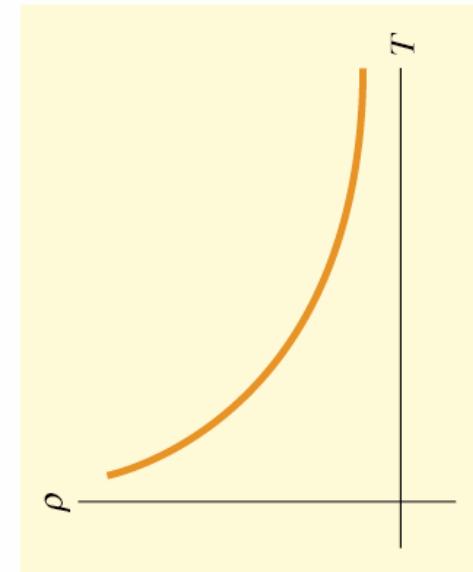
Serway, Physics for Scientists and Engineers, 5/e
Figure 27.13



Inc.

Serway, Physics for Scientists and Engineers, 5/e
Figure 27.14


Inc.

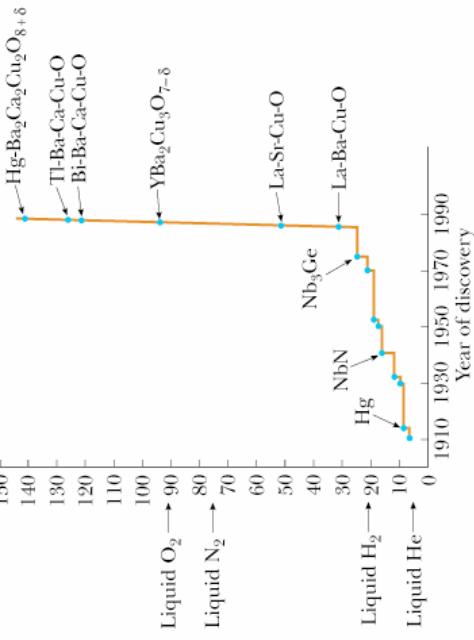

Harcourt, Inc.

Harcourt, Inc.

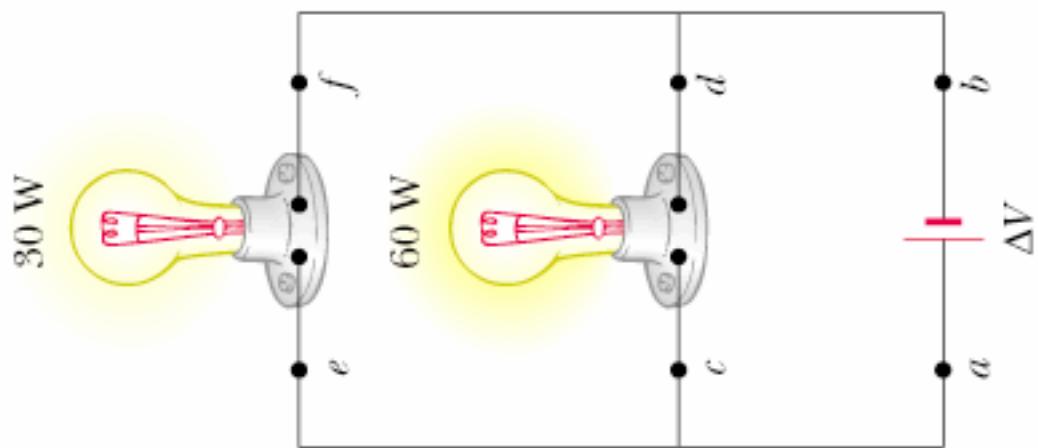Seway, Physics for Scientists and Engineers, 5/e
Figure 27.17



electromotive force


- A battery is a source of **electromotive force (emf)**. It moves charges "uphill" from a lower potential to a higher potential.
- When positive charges are moved from the negative terminal to the positive terminal, the potential increases by ϵ ,
- but since we have to work against the internal resistance r of the battery, there is a loss of potential by Ir .
- The terminal voltage of the battery:

$$\Delta V = \epsilon - Ir \quad (1)$$

- The **emf ϵ** is equal to the **open-circuit voltage**, (when the current is zero)


$$\begin{aligned}\Delta V &= IR \\ &= \epsilon - Ir \\ \epsilon &= I(R + r)\end{aligned}$$

$$I = \frac{\epsilon}{R + r}$$

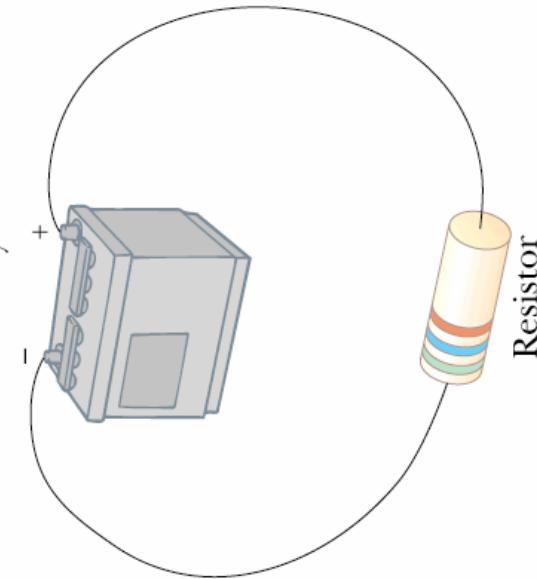

Senway, Physics for Scientists and Engineers, 5/e
Figure 28.1

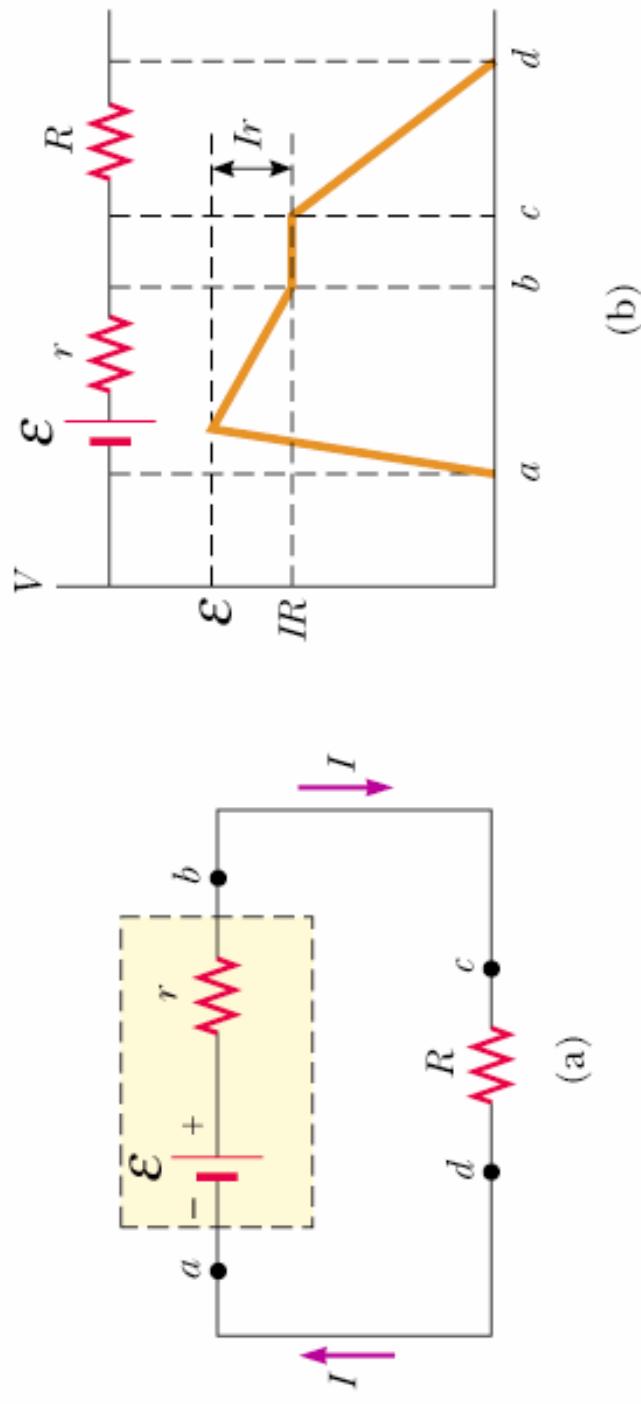Serway, Physics for Scientists and Engineers, 5/e
Figure 28.2



Electrical energy and power

- Amount of energy released when ΔQ moves across ΔV

$$\Delta U = \Delta Q \Delta V$$

- Rate at which this energy is released: **Power**

$$P = \frac{\Delta U}{\Delta t} = \frac{\Delta Q}{\Delta t} \Delta V$$

$$P = I \Delta V$$

$$P = I \Delta V = I^2 R = \frac{(\Delta V)^2}{R}$$

-

- Unit of power is **watt**: W (J s^{-1})

Combination of Resistors

Series combination

- The currents in the resistors connected in series are the same
- For a series combination total voltage ΔV ,

$$\Delta V = \Delta V_1 + \Delta V_2 \quad (10)$$

- Because the currents are the same:

$$\Delta V_1 = IR_1 \quad \Delta V_2 = IR_2 \quad (11)$$

- For a resistor equivalent to the combination;

$$\Delta V = IR_{eq} \quad (12)$$

- Substituting:




$$IR_{eq} = IR_1 + IR_2 \quad (13)$$

$$R_{eq} = R_1 + R_2 \quad (14)$$

- For a series combination of many resistors:

$$R_{eq} = R_1 + R_2 + R_3 + \dots \dots \quad (15)$$

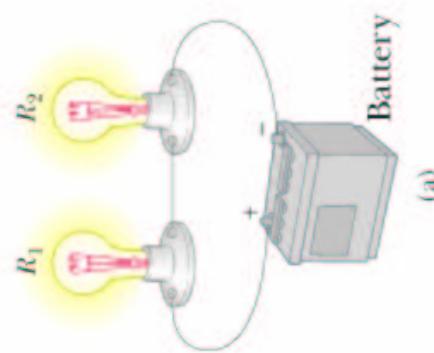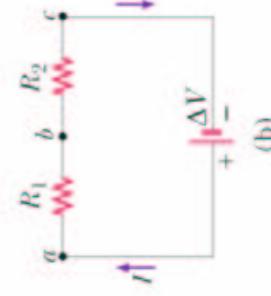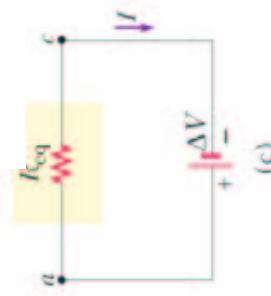- The equivalent resistance of a series combination of resistors is greater than any of the individual resistors.



Serway, Physics for Scientists and Engineers, 5/e
Figure 28.4

Parallel combination

- The individual potential differences across resistors connected in parallel are all the same and are equal to the potential difference applied across the combination.
- For a parallel combination total current,

$$I = I_1 + I_2 \quad (16)$$

- Substituting:


$$\frac{\Delta V}{R_{eq}} = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} \quad (17)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (18)$$

- For a series combination of many capacitors:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots \dots \dots \quad (19)$$

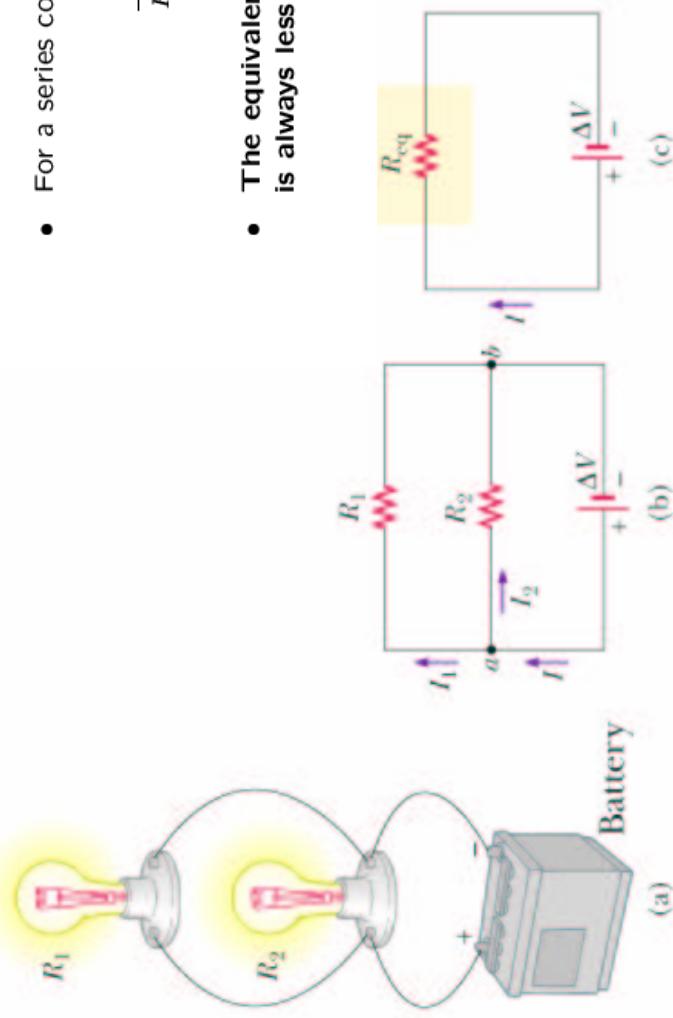
- The equivalent resistance of a parallel combination of resistors is always less than any individual resistance in the combination.



Senay, Physics for Scientists and Engineers, 5/e
Figure 28.5


- Find the resistance between a and c
- if the potential difference between a and c is 42 V, what is the current in each resistor ?

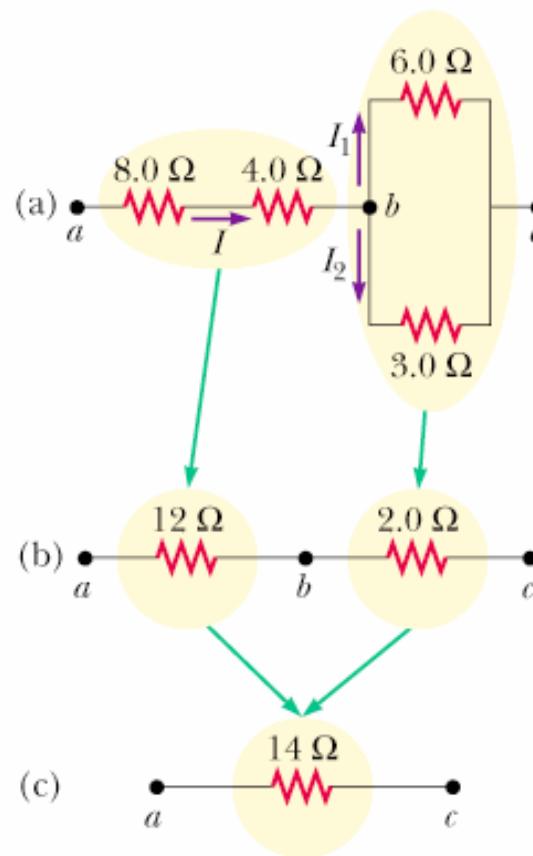Serway, Physics for Scientists and Engineers, 5/e
Figure 28.6



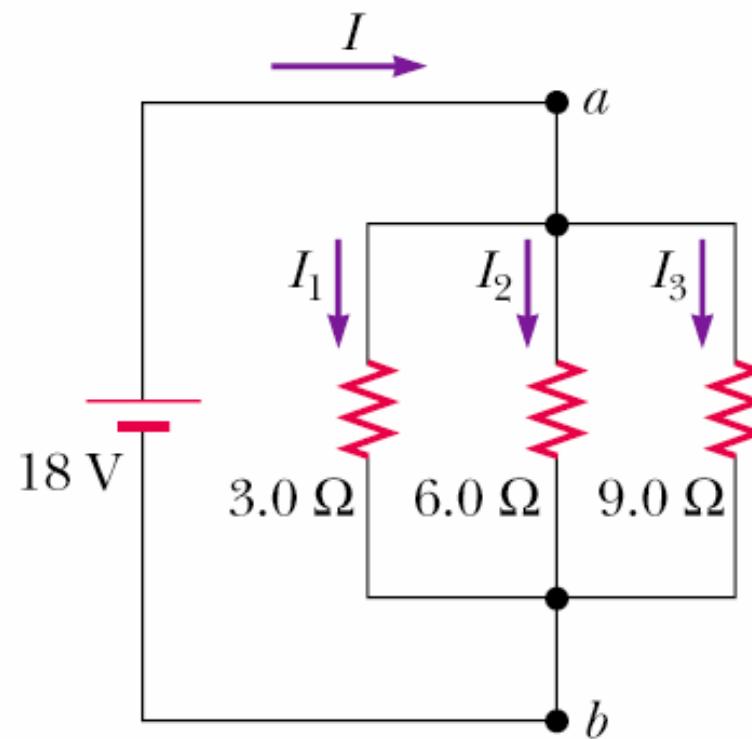- a. Find the current in each resistor
- b. Power delivered to each resistor and total power delivered
- c. Equivalent resistance

Serway, Physics for Scientists and Engineers, 5/e
Figure 28.7



Serway, Physics for Scientists and Engineers, 5/e
Figure 28.8

