

26-5)a) $r_1 = 0.4 \text{ m}$, $r_2 = 1.0 \text{ m}$, $q_{\text{total}} = 7.0 \mu\text{C}$

$\frac{q_1}{q_2} = \frac{r_1}{r_2}$, since both spheres must be at the same electric potential; see Ex 25.9.

Setting $q_2 = q_{\text{total}} - q_1 \Rightarrow \frac{q_1}{q_{\text{total}} - q_1} = 0.4 \Rightarrow \boxed{q_1 = \frac{2}{7} q_{\text{total}} = 2.0 \mu\text{C}}$
 $\Rightarrow \boxed{q_2 = 5.0 \mu\text{C}}$

26.5)b) $V_{\text{total}} = V_1 + V_2 = 2V_1$, since $V_1 = V_2$.

$V_1 = k_e \frac{q_1}{r_1} = 4.495 \text{ kV} \Rightarrow \boxed{V_{\text{total}} = 8.99 \text{ kV}}$

26-7)a) $A = 7.60 \text{ cm}^2 = 7.6 \times 10^{-4} \text{ m}^2$; $d = 1.80 \text{ mm} = 1.80 \times 10^{-3} \text{ m}$; $\Delta V = 20.0 \text{ V}$


26-7)b) $\Delta V = Ed$; $\epsilon_0 = 8.854 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$

$\Rightarrow \boxed{E = \frac{\Delta V}{d} = 11.1 \text{ kV}, \text{ towards the neg. plate}}$


$E = \frac{\sigma}{\epsilon_0} \Rightarrow \boxed{\sigma = \epsilon_0 E = 9.83 \times 10^{-8} \text{ C/m}^2}$

26-7)c) $\boxed{C = \frac{\epsilon_0 A}{d} = 3.74 \text{ pF}}$

26-7)d) $\boxed{C\Delta V = Q = 74.767 \text{ pC}}$

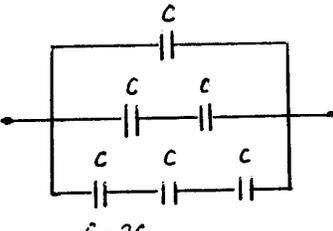26-18)  $\frac{1}{C_{eq,1}} = \frac{1}{C}$; $\frac{1}{C_{eq,2}} = \frac{1}{C} + \frac{1}{C} = \frac{2}{C} \Rightarrow \frac{1}{C_{eq,3}} = \frac{3}{C}$

$\Rightarrow \boxed{C_{eq, \text{tot}} = C + \frac{C}{2} + \frac{C}{3} = \frac{11C}{6}}$

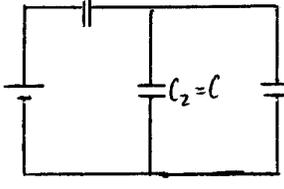26-22)a)  $\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2 + C_3} = \frac{1}{2C}$
 $\Rightarrow \boxed{C_{eq} = 2C}$

26-54(b) The potential difference across each of the two pairs in parallel is the same and is equal to 90 V.

$$\Delta V_{3.0\mu F} = \Delta V_{2.0\mu F} = 60.0V$$

$$\Delta V_{6.0\mu F} = \Delta V_{4.0\mu F} = 30.0V$$

for either upper or lower series comb!


$$\Delta V_{tot} = 90.0V = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$Q_{upper,1} = Q_{upper,2} = 180\mu C$$

$$Q_{lower,1} = Q_{lower,2} = 120\mu C$$

26-54(d) $U = \frac{1}{2} C (\Delta V)^2 = \frac{1}{2} \left(\frac{3}{10} \mu F \right) (90.0V)^2 = 13.5 mJ$

26-61(a) Figure P26.61 looks just like

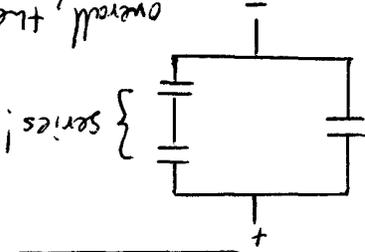


overall, the combs parallel!

$$\Rightarrow C_{total} = \frac{C_0 A K_1}{L} + \frac{C_0 \left(\frac{A}{2} \right) \left(\frac{1}{K_2} + \frac{1}{K_3} \right)}{L} \Rightarrow C_{total} = \frac{C_0 A}{L} \left(K_1 + \frac{1}{2} \left(\frac{1}{K_2} + \frac{1}{K_3} \right) \right)$$

26-61(b) Plugging in the given values yields $C_{total} = 1.76 pF$

27-24) $R_1 = 4.0 \times 10^{-3} \Omega \cdot m$, $R_2 = 6.0 \times 10^{-3} \Omega \cdot m$, $A = (3.0 \times 10^{-3} m)^2$, $l_1 = 0.25 m$, $l_2 = 0.40 m$

Figure P27.24 looks just like:

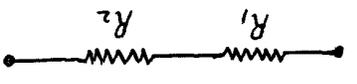

$$\Rightarrow R_{total} = \frac{1}{A} (R_1 l_1 + R_2 l_2) = 377.77 \Omega$$

27-46(a) $P = I^2 R = I^2 R_{cu} = \frac{V}{A} \cdot \frac{V}{L} = \frac{V^2}{A L} = \frac{(20.0A)^2 (1.7 \times 10^{-8} \Omega \cdot m) (1.0m)}{\pi (1.0265 \times 10^{-3} m)^2} \approx 2.05 W$

27-46(b) $R_{Al} = R_{cu} \cdot \frac{\rho_{Al}}{\rho_{cu}} = R_{cu} \cdot \frac{3.41 W}{3.41 W} = R_{cu} > R_{cu} \Rightarrow$ Copper is safer than Aluminum!

Note: Silver wiring is normally considered to be the safest (due to its low resistivity), but it is too expensive to implement in everyday circuits.

27-54(a) $R = \frac{(\Delta V)^2}{P}$; $R_1 = \frac{(120V)^2}{100W} = 144 \Omega$; $R_2 = \frac{(120V)^2}{25W} = 576 \Omega$

27-54(b) $I = \frac{\Delta V}{R} \Rightarrow \Delta t = \frac{QR}{\Delta V} = \frac{(1C)(1576 \Omega)}{120V} \Rightarrow \Delta t = 4.80 \text{ sec}$

$U = Q\Delta V \Rightarrow$ Due to the potential difference, the potential energy is lower upon exit.

27-54(c) $P = I\Delta V = \frac{U}{\Delta t} \Rightarrow \Delta t = \frac{U}{P} = \frac{1J}{25W} = 0.04 \text{ sec}$

bulbs get hot!!!

Energy enters w/current (due to $U = Q\Delta V$) and exits via emission of heat & light.

27-54(d) $\text{lost} = \frac{\$0.07}{25W} | \frac{KWh}{1000W} | \frac{\text{day}}{30 \text{ days}} | \frac{24h}{1 \text{ day}} = \1.26

The company sells energy, what else?!

(lost one SI) = $\frac{\$0.07}{KWh} | \frac{KWh}{1000W} | \frac{3600s}{h} = 1.94 \times 10^{-8} \text{ \$/J}$


28-4(a) $\xi = 12.6V$; $r = 0.08 \Omega$; $R = 5.0 \Omega$

$\xi = IR + Ir \Rightarrow I = \frac{\xi}{R+r} \Rightarrow \Delta V = IR = \frac{\xi R}{R+r} \approx 12.40V$

28-4(b) Since an add'l 35.0 A is taken from the battery, then:

$I_{new} = \frac{\xi}{R+r}$, where $I' = 35.0A$

$\Delta V = I_{new} R = 9.65V$

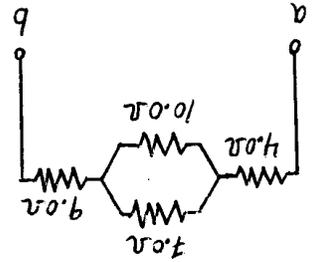

28-6(a)

$R_{eq} = 4.0 \Omega + \left(\frac{1}{\frac{1}{10.0 \Omega} + \frac{1}{4.0 \Omega}} \right) + 9.0 \Omega = \frac{291 \Omega}{17}$


28-6)b) $\Delta V = I R_{eq} \Rightarrow \boxed{I = \frac{\Delta V}{R_{eq}} = \frac{34.0V}{R_{eq}} \approx 1.99 A}$, for the 4.0Ω & 9.0Ω resistors (since current thru resistors in series is the same).

Now, the equiv. resistance of the two resistors in \parallel is $\therefore R_{eq, \parallel} = \left(\frac{1}{7.0 \Omega} + \frac{1}{10.0 \Omega} \right)^{-1} = \frac{70}{17} \Omega$

The pot. diff. (ΔV) across the two in \parallel is the same $\therefore \Delta V_{\parallel} = I R_{eq, \parallel} \approx 8.18 V$

for the 7.0Ω resistor: $I_7 = \frac{\Delta V_{\parallel}}{7.0 \Omega} \approx 1.17 A$
 for the 10.0Ω resistor: $I_{10} = \frac{\Delta V_{\parallel}}{10.0 \Omega} \approx 0.82 A$

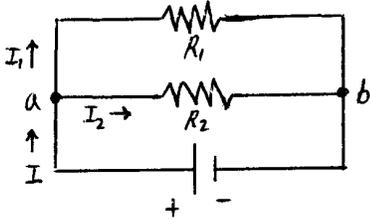28-18)a) $R_1 = 11.0 \Omega$; $R_2 = 22.0 \Omega$; $\Delta V = 33.0 V$



Two resistors in parallel $\therefore \Delta V_1 = \Delta V_2 = \Delta V$
 Using $\mathcal{P} = \frac{(\Delta V)^2}{R}$, \nearrow the fact that $R_1 < R_2$ shows that

$\mathcal{P}_1 > \mathcal{P}_2$; more power to the 11.0Ω resistor

28-18)b) $R_{eq} = \left(\frac{1}{11.0 \Omega} + \frac{1}{22.0 \Omega} \right)^{-1} \approx 7.33 \Omega$
 $\mathcal{P}_{battery} = \frac{(\Delta V)^2}{R_{eq}} = \boxed{148.5 W}$
 $\mathcal{P}_{11} = \frac{(\Delta V)^2}{11.0 \Omega} = 99 W$
 $\mathcal{P}_{22} = \frac{(\Delta V)^2}{22.0 \Omega} = 49.5 W$
 $\mathcal{P}_{battery} = \mathcal{P}_{11} + \mathcal{P}_{22} \Rightarrow \mathcal{P}_{battery} = 148.5 W$

28-18)c)
 Two resistors in series: $I_1 = I_2 = I$
 From the relation $\mathcal{P} = I^2 R$, \uparrow $\therefore R_2 > R_1$, we see that
 $\mathcal{P}_2 > \mathcal{P}_1$; 22.0Ω resistor uses more power

28-18)d) $\Delta V = I R_{eq} \Rightarrow I = \frac{33.0 V}{11.0 \Omega + 22.0 \Omega} = 1 A \Rightarrow \mathcal{P}_1 = I^2 R_1 = 11.0 W$; $\mathcal{P}_2 = I^2 R_2 = 22.0 W$
 $\mathcal{P}_{total} = \mathcal{P}_1 + \mathcal{P}_2 = \boxed{33.0 W}$
 $\mathcal{P}_{battery} = I \Delta V = (1 A)(33.0 V) = \boxed{33.0 W}$

28-18)e) $\mathcal{P}_{parallel} > \mathcal{P}_{series}$