

PHYS 232 PS 5 Solutions

P28.26 Name the currents as shown in the figure to the right. Then $w + x + z = y$. Loop equations are

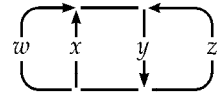


FIG. P28.26

$$\begin{aligned} -200w - 40.0 + 80.0x &= 0 \\ -80.0x + 40.0 + 360 - 20.0y &= 0 \\ +360 - 20.0y - 70.0z + 80.0 &= 0 \end{aligned}$$

Eliminate y by substitution.

$$\begin{cases} x = 2.50w + 0.500 \\ 400 - 100x - 20.0w - 20.0z = 0 \\ 440 - 20.0w - 20.0x - 90.0z = 0 \end{cases}$$

Eliminate x .

$$\begin{cases} 350 - 270w - 20.0z = 0 \\ 430 - 70.0w - 90.0z = 0 \end{cases}$$

Eliminate $z = 17.5 - 13.5w$ to obtain $430 - 70.0w - 1.575 + 1.215w = 0$

$$w = \frac{70.0}{70.0} = \boxed{1.00 \text{ A up ward in } 200 \Omega}.$$

Now $z = \boxed{4.00 \text{ A up ward in } 70.0 \Omega}$

$$x = \boxed{3.00 \text{ A up ward in } 80.0 \Omega}$$

$$y = \boxed{8.00 \text{ A down ward in } 20.0 \Omega}$$

and for the 200Ω , $\Delta V = IR = (1.00 \text{ A})(200 \Omega) = \boxed{200 \text{ V}}$.

P28.30 We apply Kirchoff's rules to the second diagram.

$$50.0 - 2.00I_1 - 2.00I_2 = 0 \quad (1)$$

$$20.0 - 2.00I_3 + 2.00I_2 = 0 \quad (2)$$

$$I_1 = I_2 + I_3 \quad (3)$$

Substitute (3) into (1), and solve for I_1 , I_2 , and I_3

$$I_1 = 20.0 \text{ A} ; I_2 = 5.00 \text{ A} ; I_3 = 15.0 \text{ A} .$$

Then apply $P = I^2R$ to each resistor:

$$(2.00 \Omega)_1 : P = I_1^2(2.00 \Omega) = (20.0 \text{ A})^2(2.00 \Omega) = \boxed{800 \text{ W}}$$

$$(4.00 \Omega) : P = \left(\frac{5.00}{2} \text{ A}\right)^2(4.00 \Omega) = \boxed{25.0 \text{ W}}$$

(Half of I_2 goes through each)

$$(2.00 \Omega)_3 : P = I_3^2(2.00 \Omega) = (15.0 \text{ A})^2(2.00 \Omega) = \boxed{450 \text{ W}} .$$

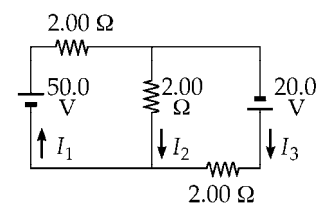
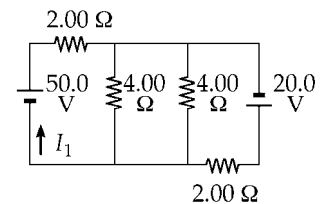


FIG. P28.30

P28.32 (a) $i(t) = -I_0 e^{-t/RC}$
 $I_0 = \frac{Q}{RC} = \frac{5.10 \times 10^{-6} \text{ C}}{(1\,300 \, \Omega)(2.00 \times 10^{-9} \text{ F})} = 1.96 \text{ A}$
 $i(t) = -(1.96 \text{ A}) \exp\left[\frac{-9.00 \times 10^{-6} \text{ s}}{(1\,300 \, \Omega)(2.00 \times 10^{-9} \text{ F})}\right] = \boxed{-61.6 \text{ mA}}$

(b) $q(t) = Q e^{-t/RC} = (5.10 \, \mu\text{C}) \exp\left[\frac{-8.00 \times 10^{-6} \text{ s}}{(1\,300 \, \Omega)(2.00 \times 10^{-9} \text{ F})}\right] = \boxed{0.235 \, \mu\text{C}}$

(c) The magnitude of the maximum current is $I_0 = \boxed{1.96 \text{ A}}$.

P28.36 (a) $\tau = RC = (1.50 \times 10^5 \, \Omega)(10.0 \times 10^{-6} \text{ F}) = \boxed{1.50 \text{ s}}$

(b) $\tau = (1.00 \times 10^5 \, \Omega)(10.0 \times 10^{-6} \text{ F}) = \boxed{1.00 \text{ s}}$

(c) The battery carries current $\frac{10.0 \text{ V}}{50.0 \times 10^3 \, \Omega} = 200 \, \mu\text{A}$.

The $100 \text{ k}\Omega$ carries current of magnitude $I = I_0 e^{-t/RC} = \left(\frac{10.0 \text{ V}}{100 \times 10^3 \, \Omega}\right) e^{-t/1.00 \text{ s}}$.

So the switch carries downward current $\boxed{200 \, \mu\text{A} + (100 \, \mu\text{A}) e^{-t/1.00 \text{ s}}}$.

P28.64 The battery supplies energy at a changing rate $\frac{dE}{dt} = P = \mathcal{E}I = \mathcal{E}\left(\frac{\mathcal{E}}{R} e^{-t/RC}\right)$.

Then the total energy put out by the battery is $\int dE = \int_0^{\infty} \frac{\mathcal{E}^2}{R} \exp\left(-\frac{t}{RC}\right) dt$

$\int dE = \frac{\mathcal{E}^2}{R} (-RC) \int_0^{\infty} \exp\left(-\frac{t}{RC}\right) \left(-\frac{dt}{RC}\right) = -\mathcal{E}^2 C \exp\left(-\frac{t}{RC}\right) \Big|_0^{\infty} = -\mathcal{E}^2 C [0 - 1] = \mathcal{E}^2 C$.

The power delivered to the resistor is $\frac{dE}{dt} = P = \Delta V_R I = I^2 R = R \frac{\mathcal{E}^2}{R^2} \exp\left(-\frac{2t}{RC}\right)$.

So the total internal energy appearing in the resistor is $\int dE = \int_0^{\infty} \frac{\mathcal{E}^2}{R} \exp\left(-\frac{2t}{RC}\right) dt$

$\int dE = \frac{\mathcal{E}^2}{R} \left(-\frac{RC}{2}\right) \int_0^{\infty} \exp\left(-\frac{2t}{RC}\right) \left(-\frac{2dt}{RC}\right) = -\frac{\mathcal{E}^2 C}{2} \exp\left(-\frac{2t}{RC}\right) \Big|_0^{\infty} = -\frac{\mathcal{E}^2 C}{2} [0 - 1] = \frac{\mathcal{E}^2 C}{2}$.

The energy finally stored in the capacitor is $U = \frac{1}{2}C(\Delta V)^2 = \frac{1}{2}C\varepsilon^2$. Thus, energy of the circuit is conserved $\varepsilon^2 C = \frac{1}{2}\varepsilon^2 C + \frac{1}{2}\varepsilon^2 C$ and resistor and capacitor share equally in the energy from the battery.

- *P28.68** (a) With the switch closed, current exists in a simple series circuit as shown. The capacitors carry no current. For R_2 we have

$$P = I^2 R_2 \quad I = \sqrt{\frac{P}{R_2}} = \sqrt{\frac{2.40 \text{ V} \cdot \text{A}}{7000 \text{ V/A}}} = 18.5 \text{ mA} .$$

The potential difference across R_1 and C_1 is

$$\Delta V = IR_1 = (1.85 \times 10^{-2} \text{ A})(4000 \text{ V/A}) = 74.1 \text{ V} .$$

The charge on C_1

$$Q = C_1 \Delta V = (3.00 \times 10^{-6} \text{ C/V})(74.1 \text{ V}) = \boxed{222 \mu\text{C}} .$$

The potential difference across R_2 and C_2 is

$$\Delta V = IR_2 = (1.85 \times 10^{-2} \text{ A})(7000 \Omega) = 130 \text{ V} .$$

The charge on C_2

$$Q = C_2 \Delta V = (6.00 \times 10^{-6} \text{ C/V})(130 \text{ V}) = 778 \mu\text{C} .$$

The battery emf is

$$\mathcal{E} = I(R_1 + R_2) = 1.85 \times 10^{-2} \text{ A}(4000 + 7000) \text{ V/A} = 204 \text{ V} .$$

- (b) In equilibrium after the switch has been opened, no current exists. The potential difference across each resistor is zero. The full 204 V appears across both capacitors. The new charge C_2

$$Q = C_2 \Delta V = (6.00 \times 10^{-6} \text{ C/V})(204 \text{ V}) = 1222 \mu\text{C}$$

for a change of $1222 \mu\text{C} - 778 \mu\text{C} = \boxed{444 \mu\text{C}} .$

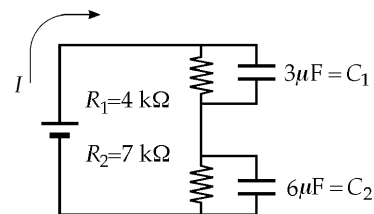


FIG. P28.68(a)

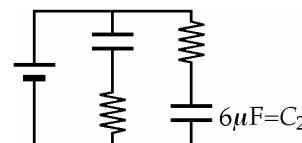


FIG. P28.68(b)

- P28.75** The total resistance between points b and c is:

$$R = \frac{(2.00 \text{ k}\Omega)(3.00 \text{ k}\Omega)}{2.00 \text{ k}\Omega + 3.00 \text{ k}\Omega} = 1.20 \text{ k}\Omega .$$

The total capacitance between points d and e is:

$$C = 2.00 \mu\text{F} + 3.00 \mu\text{F} = 5.00 \mu\text{F} .$$

The potential difference between point d and e in this series RC circuit at any time is:

$$\Delta V = \mathcal{E} \left[1 - e^{-t/RC} \right] = (120.0 \text{ V}) \left[1 - e^{-1000t/6} \right] .$$

Therefore, the charge on each capacitor between points d and e is:

$$q_1 = C_1 \Delta V = (2.00 \mu\text{F})(120.0 \text{ V}) \left[1 - e^{-1000t/6} \right] = \boxed{(240 \mu\text{C}) \left[1 - e^{-1000t/6} \right]}$$

$$\text{and } q_2 = C_2 (\Delta V) = (3.00 \mu\text{F})(120.0 \text{ V}) \left[1 - e^{-1000t/6} \right] = \boxed{(360 \mu\text{C}) \left[1 - e^{-1000t/6} \right]} .$$

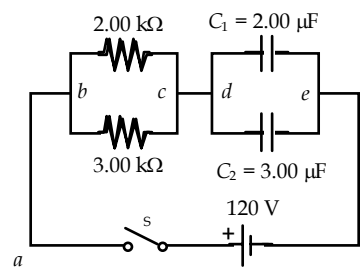


FIG. P28.75