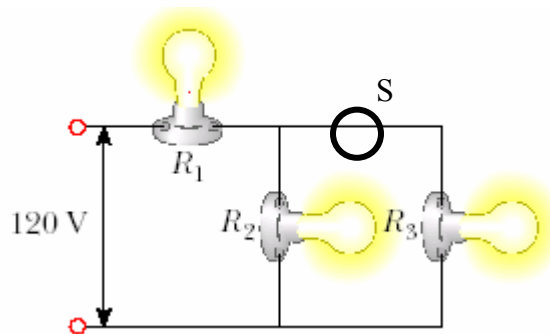


232 Lecture supplement 12

- 67.** Three 60.0-W, 120-V lightbulbs are connected across a 120-V power source, as shown in Figure P28.67. Find
- the total power delivered to the three bulbs and
 - the voltage across each. Assume that the resistance of each bulb is constant (even though in reality the resistance might increase markedly with current).
 - Now the switch S is opened. Compare the brightness of bulbs R₁, R₂ and R₃ before and after the switch is opened.



- P28.67** (a) First determine the resistance of each light bulb: $P = \frac{(\Delta V)^2}{R}$
- $$R = \frac{(\Delta V)^2}{P} = \frac{(120 \text{ V})^2}{60.0 \text{ W}} = 240 \ \Omega .$$
- We obtain the equivalent resistance R_{eq} of the network of light bulbs by identifying series and parallel equivalent resistances:
- $$R_{\text{eq}} = R_1 + \frac{1}{(1/R_2) + (1/R_3)} = 240 \ \Omega + 120 \ \Omega = 360 \ \Omega .$$

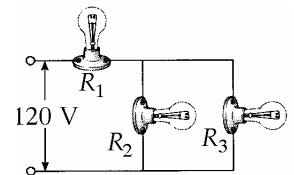


FIG. P28.67

The total power dissipated in the 360 Ω is

$$P = \frac{(\Delta V)^2}{R_{\text{eq}}} = \frac{(120 \text{ V})^2}{360 \ \Omega} = \boxed{40.0 \text{ W}} .$$

- (b) The current through the network is given by $P = I^2 R_{\text{eq}}$:

$$I = \sqrt{\frac{P}{R_{\text{eq}}}} = \sqrt{\frac{40.0 \text{ W}}{360 \ \Omega}} = \frac{1}{3} \text{ A} .$$

The potential difference across R_1 is

$$\Delta V_1 = IR_1 = \left(\frac{1}{3} \text{ A} \right) (240 \ \Omega) = \boxed{80.0 \text{ V}} .$$

The potential difference ΔV_{23} across the parallel combination of R_2 and R_3 is

$$\Delta V_{23} = IR_{23} = \left(\frac{1}{3} \text{ A}\right) \left(\frac{1}{\left(\frac{1}{240 \Omega}\right) + \left(\frac{1}{240 \Omega}\right)}\right) = \boxed{40.0 \text{ V}}.$$

You can also determine ΔV_{23} by using:

$$\begin{aligned} 120 \text{ V} &= \Delta V_{23} + \Delta V_1 \\ \Rightarrow \Delta V_{23} &= 120 - 80 = 40 \text{ V} \end{aligned}$$

(c) The power dissipated in each bulb before S is opened:

$$P_1 = \frac{(\Delta V_1)^2}{R_1} = \frac{80^2}{240} \text{ W} = 26.67 \text{ W}$$

$$P_2 = P_3 = \frac{(\Delta V_{23})^2}{R_2} = \frac{40^2}{240} \text{ W} = 6.67 \text{ W}$$

When the switch is opened R3 is off. Now R1 and R2 are in series and the equivalent resistance is $R_1 + R_2 = 480 \Omega$. And the current through both bulbs:

$$I = \frac{\Delta V}{R_{eq}} = \frac{120}{480} = 0.25 \text{ A}$$

So now the new potential differences and power dissipated for R1 and R2:

$$\Delta V_1 = IR_1 = 0.25 \cdot 240 = 60 \text{ V}$$

$$\Delta V_2 = IR_2 = 0.25 \cdot 240 = 60 \text{ V}$$

$$P_1 = P_2 = \frac{(\Delta V_1)^2}{R_1} = \frac{(\Delta V_2)^2}{R_2} = \frac{60^2}{240} \text{ W} = 15 \text{ W}$$

So when S is opened R1 becomes less bright while R2 becomes brighter.