

Lecture Supplement 25: Solution for 32.26

P32.26 (a) $I = \frac{\varepsilon}{R} = \frac{12.0 \text{ V}}{12.0 \Omega} = \boxed{1.00 \text{ A}}$

(b) Initial current is 1.00 A: $\Delta V_{12} = (1.00 \text{ A})(12.00 \Omega) = \boxed{12.0 \text{ V}}$
 $\Delta V_{1200} = (1.00 \text{ A})(1200 \Omega) = \boxed{1.20 \text{ kV}}$
 $\Delta V_L = \boxed{1.21 \text{ kV}}$.

(c) $I = I_{\text{max}} e^{-R\tau/L}$: $\frac{dI}{dt} = -I_{\text{max}} \frac{R}{L} e^{-R\tau/L}$
 and $-L \frac{dI}{dt} = \Delta V_L = I_{\text{max}} R e^{-R\tau/L}$.
 Solving $12.0 \text{ V} = (1.212 \text{ V}) e^{-1212\tau/2.00}$
 so $9.90 \times 10^{-3} = e^{-606\tau}$.
 Thus, $\boxed{t = 7.62 \text{ ms}}$.

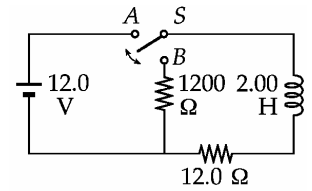


FIG. P32.26