

28-6

only 1 Loop

$$i) I = \mathcal{E} / (R + r)$$

$$320 \times 10^{-3} A = \mathcal{E} / (18.5 \Omega + 2.25 \Omega)$$

$$\boxed{\mathcal{E} = 6.00 V}$$


$$ii) V_{\text{terminal}}$$

$$V_{\text{term}} = \mathcal{E} - Ir = 6.00 V - (320 \times 10^{-3} A)(0.25 \Omega)$$

$$\boxed{V_{\text{term}} = 5.92 V}$$

28-17

a)

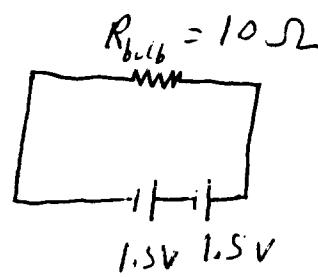


$$I_o = \frac{2E}{R} = \frac{2(1.5V)}{10\Omega} = 0.30A$$

All power is dissipated Through R_{bulb}

$$P_o = I_o^2 R = (0.30A)^2 (10\Omega) = 0.90W$$

b)

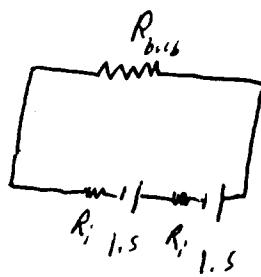

$$P = I^2 R$$

$$\frac{2}{3}(0.90W) = I^2 (10\Omega)$$

$$I = 0.25A$$

\therefore For a single Loop

$$I = \frac{2E}{R+2r}$$

$$0.25A = \frac{2(1.5V)}{10\Omega + 2r}$$

$$r = 1.0\Omega / \text{battery}$$

28 - 34

Reduce To Single Loop

1) combine R_3 & R_5





$$\frac{1}{R_6} = \frac{1}{R_3} + \frac{1}{R_5} = \frac{1}{3\Omega} + \frac{1}{6\Omega}$$

$$R_6 = 2\Omega$$

2) Combine R_2 , R_6 , and R_x

$$R_Z = R_2 + R_6 + R_x = 4\Omega + R_x$$

$(2\Omega + 2\Omega + R_x)$ ↗

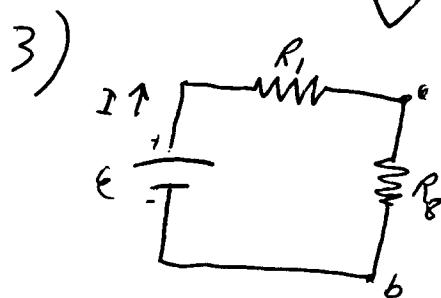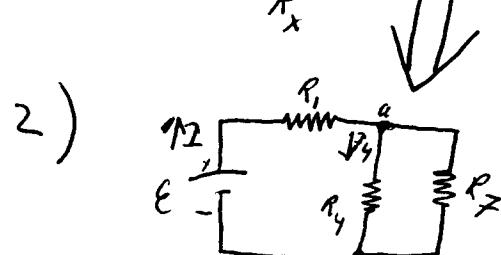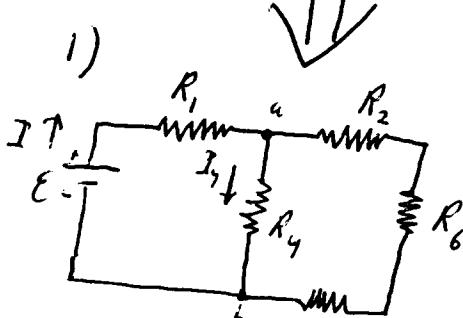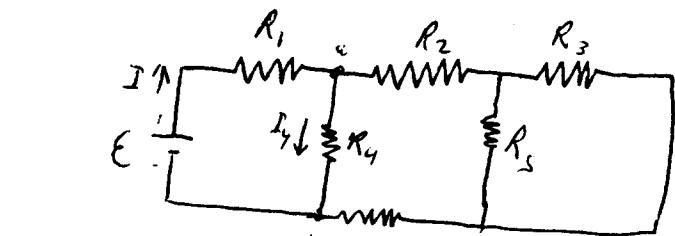

3) Combine R_4 and R_Z

$$\frac{1}{R_8} = \frac{1}{R_4} + \frac{1}{R_Z} = \frac{1}{4\Omega} + \frac{1}{4\Omega + R_x}$$

$$R_8 = \left(\frac{16 + 4R_x}{8 + R_x} \right) \Omega$$

4) Find current in single loop

$$I = \frac{E}{(R_1 + R_8)} \Rightarrow \frac{24V}{1\Omega + \left(\frac{16 + 4R_x}{8 + R_x} \right) \Omega}$$

$$= \frac{24(8 + R_x)}{24 + 5R_x} A$$

(Continued on next page)

28-34 cont.

5) Use The Voltage across R_8 and across R_4

$$V_{ab} = IR_8 = I_4 R_4$$

$$\left(\frac{24(8 + R_x)}{24 + 5R_x} \right) \left(\frac{16 + 4R_x}{8 + R_x} \right) = I_4 (4\Omega)$$

Solve for I_4


$$I_4 = \frac{24(4 + R_x)}{24 + 5R_x}$$

6) find The power dissipated Through R_4

$$P_4 = I_4^2 R_4 \\ = \left(\frac{24(4 + R_x)}{24 + 5R_x} \right)^2 4\Omega =$$

$$P_4 = \left[\frac{48(4 + R_x)}{24 + 5R_x} \right]^2 W$$

28-37

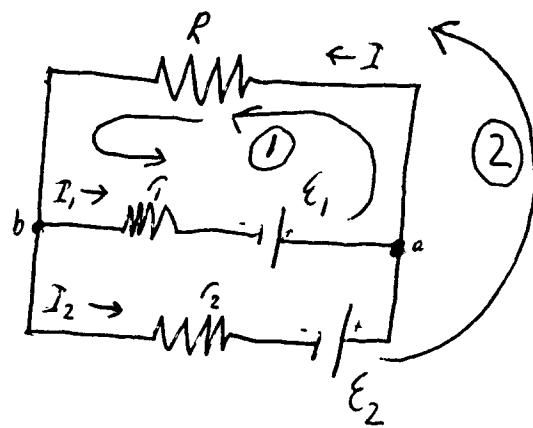

From conservation of current $I = I_1 + I_2 = 0$

$$\text{Loop 1: } E_1 - I_1 R - IR = 0$$

$$+12V - I_1 (0.1\Omega) - I (5\Omega) = 0$$

$$\text{Loop 2: } E_2 + I_2 R - IR = 0$$

$$+10 - I_2 (10\Omega) - I (5\Omega) = 0$$

Solve:

$$\underline{I_1 = 2.52A} \quad \underline{I_2 = -0.17A} \quad \underline{I = 2.35A}$$

\therefore Current Through R is $2.35A$

E_1 supplies $2.52A$

E_2 supplies No Current

(it's being charged by E_1)

27-49

$$E = \langle k, E \rangle = \frac{3}{2} k T$$

$$\text{Si: } (1.1 \text{ eV})(1.6 \times 10^{-19} \text{ J/eV}) = \frac{3}{2} (1.38 \times 10^{-23} \text{ J/K}) T_{S_i}$$

$$T_{S_i} = 8.5 \times 10^3 \text{ K}$$

$$G_e: (0.7 \text{ eV})(1.6 \times 10^{-19} \text{ J/eV}) = \frac{3}{2} (1.38 \times 10^{-23} \text{ J/K}) T_{G_e}$$

$$T_{G_e} = 5.4 \times 10^3 \text{ K}$$

$$(6.0 \text{ eV})(1.6 \times 10^{-19} \text{ J/eV}) = \frac{3}{2} (1.38 \times 10^{-23} \text{ J/K}) T_C$$


$$T_C = 4.6 \times 10^4 \text{ K}$$

28-47

$$V_{\text{meter}} = I_G R_G = I_S R_S \quad R_G/R_S = I_S/I_G$$

$$I = I_G + I_S = I_G \left[1 + \frac{I_S}{I_G} \right] = I_G \left[1 + \frac{R_G}{R_S} \right]$$

28-59

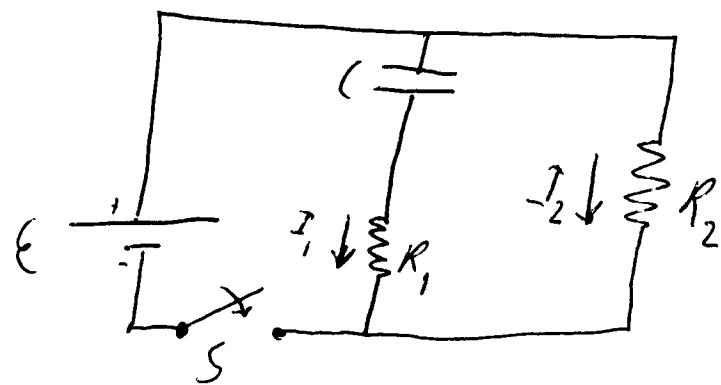

Current in R_2 is constant;

$$I_2 = \frac{\epsilon}{R_2}$$

The charging current in the capacitor branch is:

$$I_1 = \frac{\epsilon}{R_1} e^{-t/R_1 C}$$

So the current in the battery is

$$I_{\text{battery}} = I_1 + I_2 = \left(\frac{\epsilon}{R_1}\right) e^{-t/R_1 C} + \left(\frac{\epsilon}{R_2}\right)$$