
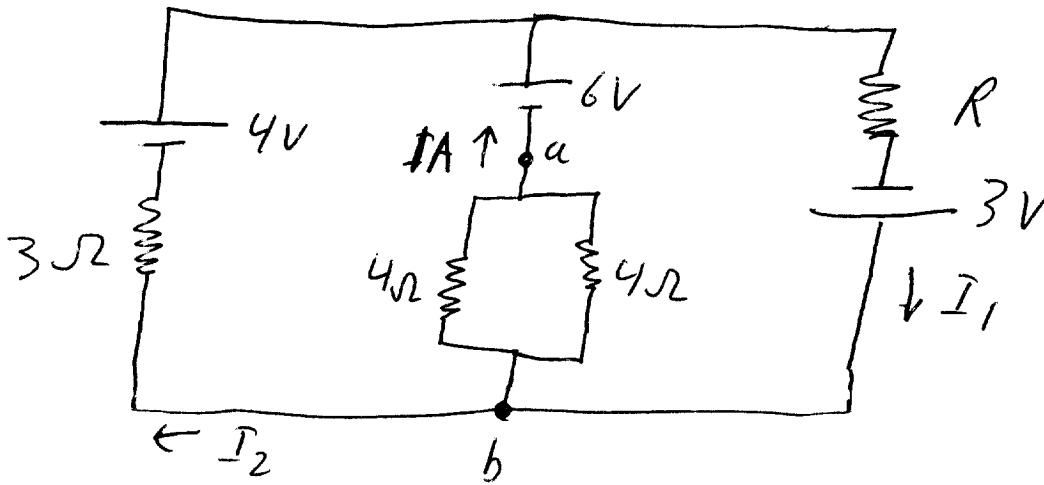


# Exam '98

1) Redraw circuit

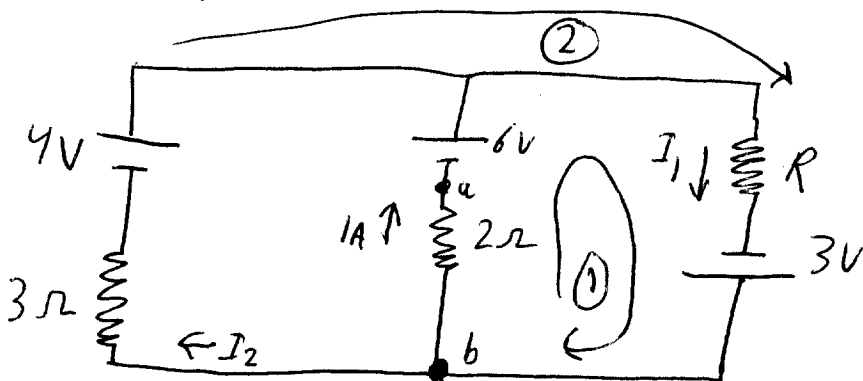

Simplify



a)  $V = IR = (1A)(2\Omega) = \boxed{2V}$

b)  $\boxed{I_2 = I_1 - 1A}$  or  $I_2 + I_1 = -1A$   
or  $I_2 + 1A = I_1$

((Continued on next page))

1c) Loop 1

$$6V - RI_1 + 3V - 2\Omega(1A) = 0$$

$$6V + 3V - 2V - RI_1 = 0$$

$$7V - RI_1 = 0$$

$$RI_1 = 7V$$

$$R = 7V/I_1$$

$$I_1 = 7V/R$$

Loop 2

$$4V - RI_1 + 3V - 3I_2^* = 0$$

$$* I_2 = I_1 - 1A$$

$$4V + 3V - 3I_1 + 3V - RI_1 = 0$$

$$10V - I_1(R + 3\Omega) = 0$$


$$I_1 = \frac{10V}{R + 3\Omega}$$

$$I_1 = 1A$$

$$R = 7\Omega$$

2) a)  $F = 0$

b)

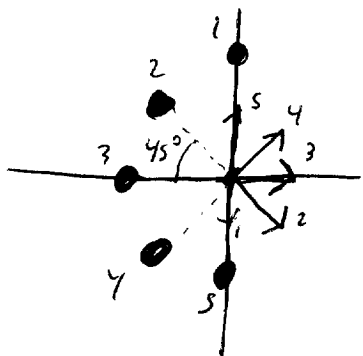

$$F = q \sum E$$

$$F_y = 0 = q[E_1 + E_5 + E_{2y} + E_{4y}]$$

$$F_x = q[E_3 + E_{4x} + E_{2x}]$$

$$\therefore F = F_x$$

$$E_{4x} = E_{2x} \quad \therefore F_x = q[E_3 + 2E_{2x}]$$

$$F_x = kq \left[ \frac{q_3}{R^2} + 2 \left( \frac{q_2}{R^2} \cos 45^\circ \right) \right]$$

$$F_x = \frac{(9 \times 10^9)(8 \times 10^{-6})}{0.01} \left[ (1 \times 10^{-6}) + 2(1 \times 10^{-6}) \cos 45^\circ \right]$$

$$F_x = 1.738 \approx 1.74 \text{ N in the } \hat{x} \text{ direction} \\ (0^\circ \text{ relative to the x-axis})$$

3)

a)  $mq = F = qE$

$q < 0$

$a = \frac{-qE}{m}$       $E = \frac{+\sigma}{2\epsilon_0}$

$a = \frac{-q\sigma}{2m\epsilon_0}$

$v = v_0 + at$

$v = v_{0x} - \frac{q\sigma}{2m\epsilon_0} t = v_{0x} - \frac{q\sigma}{2m\epsilon_0} \frac{2m\epsilon_0 v_{0x}}{q\sigma}$

$= v_{0x} - v_{0x} = 0$

$v_x(t) = 0$

b)  $x = v_0 t + \frac{1}{2} at^2$

$x = v_{0x} \left( \frac{2\epsilon_0 m v_{0x}}{q\sigma} \right) - \frac{1}{2} \frac{q\sigma}{2m\epsilon_0} \frac{4\epsilon_0^2 m^2 v_{0x}^2}{q^2 \sigma^2}$

$x = \frac{2 v_{0x}^2 \epsilon_0 m}{q\sigma} - \frac{v_{0x}^2 \epsilon_0 m}{q\sigma} = \frac{v_{0x}^2 m \epsilon_0}{q\sigma}$

$x(t) = \frac{v_{0x}^2 m \epsilon_0}{q\sigma}$

Continued on next page

3C)

$$E = \frac{q}{\epsilon_0}$$

$$q < 0$$

$$a = \frac{-q\sigma}{\epsilon_0 m}$$

$$KE_i = PE_f$$

$$\frac{1}{2} m v_{ox}^2 = m a x$$


$$\frac{1}{2} v_{ox}^2 = \frac{q\sigma x}{\epsilon_0 m}$$

$$\sigma = \frac{\epsilon_0 m v_{ox}^2}{2 q x}$$

$$\sigma = \frac{(8.85 \times 10^{-12}) (9.11 \times 10^{-31}) (1.0 \times 10^6)^2}{2 (1.6 \times 10^{-19}) (1 \times 10^{-3})}$$

$$\sigma = 2.52 \times 10^{-8} \text{ C/m}^2$$

4)

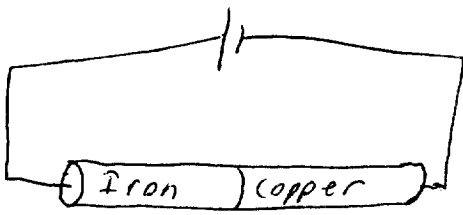

$$S = \frac{RA}{L}$$

$$a) A = \pi \times 10^{-6} \text{ m}^2$$

$$R_{Fe} = 0.318 \Omega$$

$$R_{Cu} = 0.054 \Omega$$

$$R_T = R_{Fe} + R_{Cu} = 0.3725 \Omega$$

$$b) P = I_T^2 R_T$$

$$R_T = R_{Fe} + R_{Cu} = 0.3725 \Omega$$

$$V = IR \quad I = V/R = 100V / 0.37 \Omega = 268.5 \text{ A}$$

$$P = I^2 R = (268.5 \text{ A})^2 (0.37 \Omega) = 26,851.2 \text{ W}$$

$$P = 2.69 \times 10^4 \text{ Watts}$$

(continued on next page)

4 (c) max power?

$$P = V^2 / R$$

$$R_{||T} = 4.7 \times 10^{-2} \Omega$$

$$P_{||} = (100V)^2 / 4.7 \times 10^{-2} \Omega = 2.11 \times 10^5 \text{ Watts}$$

$$P_{\text{series}} < P_{||}$$

Connect in || to maximize power loss

$$\underline{AP = 1.848 \approx 1.85 \text{ Watts}}$$