


## Week 2 (Beginning Sept 13)

**Prob2749:** If you treat electrons as a gas of independent particles, at what temperatures would an average electron have sufficient energy to cross the energy gap for silicon (1.1 eV), germanium (0.7 eV), and carbon (6 eV) ?


**Prob2806.** A flashlight battery with an internal resistance of  $0.25 \Omega$  produces a 320-mA current through a  $18.5 \Omega$  resistor. What is the emf of the battery? What is the terminal voltage of the battery in this usage?

**Prob2817.** A flashlight consists of two 1.5-V batteries connected in series to a bulb with resistance  $10 \Omega$ . (a) What is the power delivered to the bulb? (b) Batteries run down when they acquire an (internal) resistance. How large is the additional resistance if the power delivered to the bulb has decreased by one-third of its initial value?

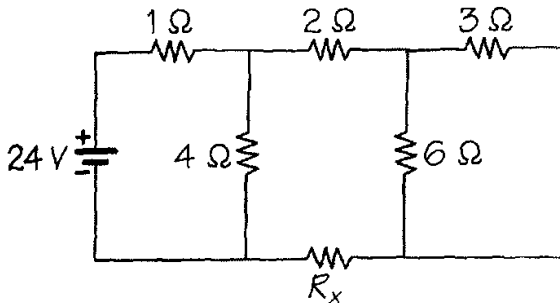
**Prob2834:** Consider the circuit shown below. Calculate the current and the power dissipated in the  $4 \Omega$  resistor as a function of the unknown resistance  $R_x$ .



**Prob2837:** Two batteries are connected in parallel as in Figure below and supply current to a load resistor of  $5 \Omega$ . One of the batteries is freshly charged, with an emf of  $\epsilon_1 = 12 \text{ V}$  and an internal resistance of  $r_1 = 0.1 \Omega$ . The other one is almost dead, with an emf of  $\epsilon_2 = 10 \text{ V}$  and an internal resistance of  $r_2 = 10 \Omega$ . What is the current through the load resistor? How much of this current is supplied by each of the batteries?

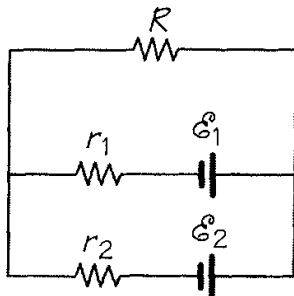

**Prob2847:** Suppose that the current to be measured by an ammeter is so large that a galvanometer deflected by the current would be pinned at its maximum reading. This problem can be resolved by the use of a shunt resistor (see figure). Show with the shunt resistor (resistance  $R_s$ ) present, the current  $I$  is given in terms of a reduced current  $I_G$  flowing through the galvanometer by the formula  $I = I_G[1 + (R_G/R_s)]$ , where  $R_G$  is the resistance of the galvanometer. Thus, a reading of the reduced current  $I_G$  allows us to determine the current  $I$ .

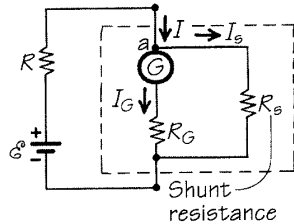

**Prob2859:** Calculate the current in the battery as a function of time for the circuit shown in the figure below if the switch  $S$  is closed at time  $t=0$ .

