

## Oscillations in Circuits

The example above leads us directly to the case of a circuit with bot L & C in it.

Before we consider this let discuss the simpler circuit with just L & R.

Applying the loop rule on the above circuit we can write:

$$E - L \frac{dI}{dt} - IR = 0. \text{ This is a differential equation in } I \text{ with the}$$

independent variable as  $t$

Try the solution to this equation as:

$$I \sim e^{-t(L/R)} + C \quad \text{therefore} \quad \frac{dI}{dt} = -\left(\frac{R}{L}\right) e^{-t(L/R)}. \text{ Hence the differential equation becomes}$$

$$\frac{E}{R} - \frac{L}{R} \left(\frac{-R}{L}\right) e^{-t(L/R)} - e^{-t(L/R)} - c = 0 \Rightarrow c = \left(\frac{E}{R}\right)$$

and

$$I = \frac{E}{R} e^{-t(L/R)} \rightarrow \text{decay of current.}$$

$$I = \frac{E}{R} \left(1 - e^{-t(L/R)}\right) \quad \text{for charging.}$$

$$t \sim RC$$

Note the parallel's between RC & RL circuits. In RC circuits the time constant  $t \sim RC$  and in

$$\text{RL circuits } t \sim \left(\frac{L}{R}\right).$$



Oscillations: Circuit w/ both L & C.

Count voltage in the direction of current

$$-L \frac{dI}{dt} - \frac{Q}{C} = 0$$

How to solve this equation:
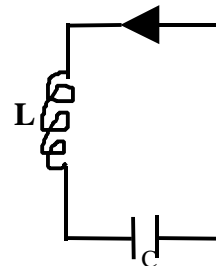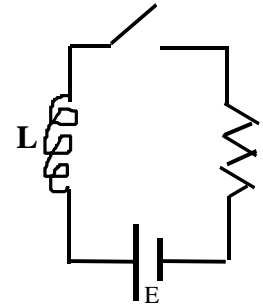
$$\frac{Q}{C} + L \frac{d^2Q}{dt^2} = 0$$



This equation reminds us of S.H.M.  $kx + m \frac{d^2x}{dt^2} = 0$

Therefore  $\omega = \sqrt{\frac{k}{m}}$  and  $x = x_0 \cos(\omega t + \phi)$ . Therefore  $\omega = \sqrt{\frac{1}{LC}}$

The charge on the capacitor (i.e. analog of  $x$ ) oscillates:

$Q = Q_0 \cos(\omega t + \phi)$ ;  $Q_0$  and  $\phi$  are determined by initial conditions.

Also,  $I = dQ/dt = -Q_0 \omega \sin(\omega t + \phi)$

Or  $I = I_0 \sin(\omega t + \phi) \rightarrow$  same frequency.

**Physical picture:** Start with capacitor charged one way and close switch - current flows into L & flows to neutralize charges on capacitor - when  $V$  is zero  $I$  has reached a maximum value -  $I$  decays  $\Rightarrow$  EMF is opposite  $\Rightarrow$  charge flows in the same direction.

Since  $L$  &  $C$  are in parallel the voltages  $V_L$  &  $V_C$  are same.

Energy in the oscillating circuits: (No resistance):

$$Q = Q_0 \cos \omega t$$

$$I = \frac{dQ}{dt} = -\omega Q_0 \sin \omega t$$

But energy in a capacitor is:


$$U_C = \frac{Q^2}{2C} = \frac{Q_0^2}{2C} \cos^2 \omega t; U_C^{\max} = \frac{Q_0^2}{2C}$$

The energy in the inductor is:

$$U_L = \frac{1}{2} L I^2 = \frac{1}{2} L \omega^2 Q_0^2 \sin^2 \omega t$$

Total  $U = U_C + U_L$  or
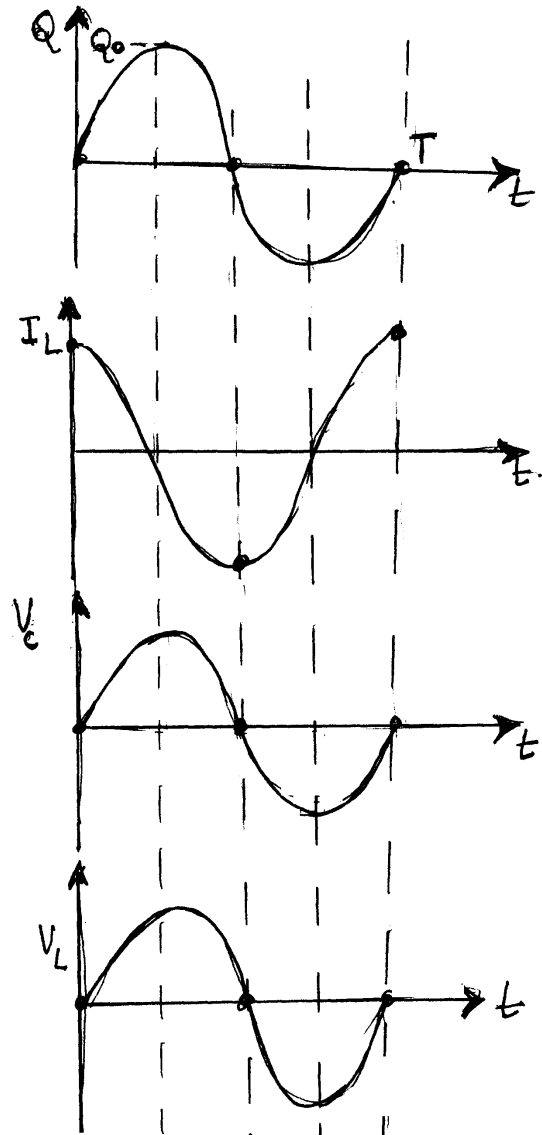
$$U = \frac{Q_0^2}{2C} (\cos^2 \omega t + \sin^2 \omega t) = \frac{Q_0^2}{2C}$$



**Damped Oscillations:** Add a resistor → real world circuits always have them:


$$-L \frac{dI}{dt} = IR - \frac{Q}{C} = 0. \text{ because of current going } \leftarrow \text{ positive charges are flowing into C.}$$

Similar to damped mechanical oscillator with drag force i.e.

$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = 0.$$

Solution is:  $Q = Q_0 e^{-at} \cos(\omega t + \phi)$ . Substituting this we find  $a = \frac{R}{2L}$  and
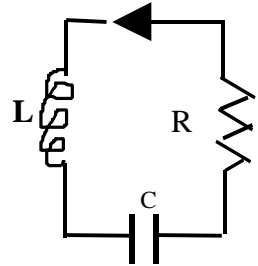
$$\omega^2 = \frac{1}{LC} - \frac{R^2}{4L^2} = \omega^2 - a^2$$



Note that something happens when  $\omega^2 - a^2$  i.e. when  $R = R_c = 2\sqrt{\frac{L}{C}}$  the circuit is damped or there is "critical damping".