

# Solutions

## QUIZ 1 - 1999

(1) A copper wire and an iron wire of the same length,  $L = 10$  meters, and diameter,  $d = 2.0$  mm are joined together in series and a potential difference of  $100$  V is applied between the ends of the composite wire [ $\rho_{\text{iron}} = 1.0 \times 10^{-7} \Omega\text{-m}$  and  $\rho_{\text{Cu}} = 1.7 \times 10^{-8} \Omega\text{-m}$ ]. Find:

(a) the total resistance in the composite wire (8 points).

$$R_{\text{Cu}} = \frac{(1.7 \times 10^{-8} \Omega\text{-m})(10)}{\frac{\pi}{4}(2)^2 \times 10^{-6}} = 54 \text{ m}\Omega$$
$$R_{\text{Fe}} = 318 \text{ m}\Omega \Rightarrow R_{\text{total}} = 372 \text{ m}\Omega$$

(b) the power dissipated in each wire (8 points)

$$P_{\text{Cu}} = I^2 R_{\text{Cu}} = \frac{(100)^2}{(0.372)^2} \cdot 54 \times 10^{-3} = 3.9 \text{ kW}$$

$$P_{\text{Fe}} = I^2 R_{\text{Fe}} = 23.0 \text{ kW}$$

$$P_{\text{total}} = 26.9 \text{ kW}$$


(c) Given the two pieces of wire separately would you connect them in series or in parallel to maximize the power dissipated? Calculate the difference in the power dissipated (6+3 points)?

$$\text{Parallel} \Rightarrow P_{\text{total}} = \frac{(100)^2}{R_{\text{Cu}}} + \frac{(100)^2}{R_{\text{Fe}}}$$
$$= 185 \text{ kW} + \cancel{26.9} 31.4 \text{ kW}$$
$$P_{\text{total}} = 216.4 \text{ kW}$$

$$\boxed{\text{Diff} = 189.5 \text{ kW}}$$

(2) Three identical charges  $q_1=q_2=q_3 = +10 \mu\text{C}$  and a fourth charge  $q_4 = -10 \mu\text{C}$  are fixed at the corners of a square of side  $a = 10 \text{ cm}$ . A test charge  $Q = 20 \mu\text{C}$  is placed at the center of the square. [ Given  $k=(4\pi\epsilon_0)^{-1}=9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$  ]

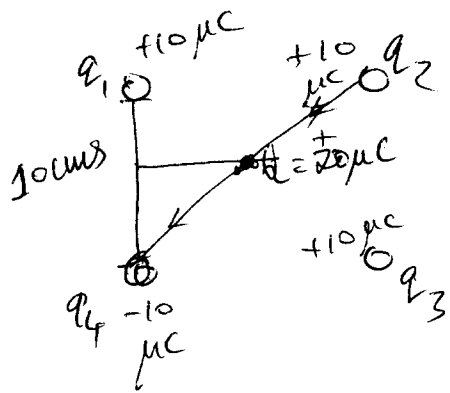(a) What is the magnitude and the direction of the electric force on  $Q$  ? (15 points)




$$F_{\text{total}} = \frac{(20 \times 20) \times 10^{-6} \times 10^{-6} \times 9 \times 10^9}{(\sqrt{2} \times 5)^2 \times 10^{-4}}$$

$$|\vec{F}| = \frac{18 \times 10000}{25} = \underline{\underline{720 \text{ N}}}$$

Direction is along diagonal.  
line connecting  $q_4$  and  $Q$ .

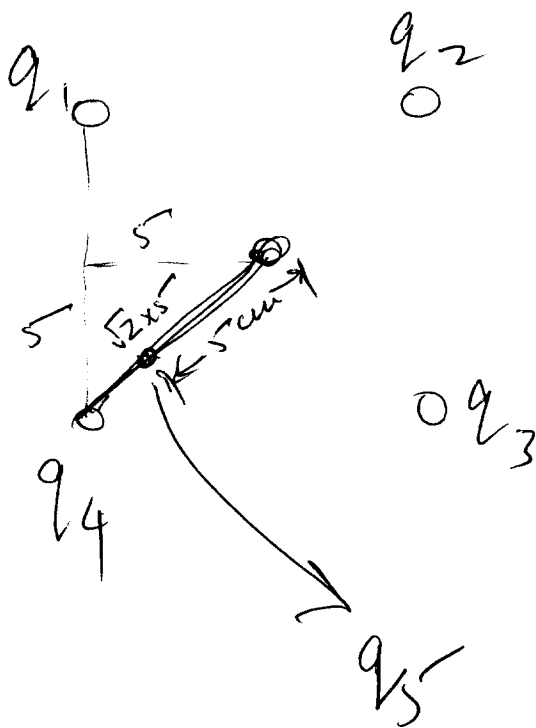(b) You are given an additional charge  $q_5 = +10 \mu\text{C}$ . Where would you place this charge such that the net force on  $Q$  is zero? (10 points).



$$\frac{2}{(\sqrt{2} \times 5)^2} = \frac{1}{r^2}$$

or  $r = 5 \text{ cm}$   
away from  $Q$   
on the line between  
 $Q$  &  $q_4$