

Prob3431: Given a series RLC circuit with $R=500 \Omega$, $L=92 \text{ mH}$, $C=2 \mu\text{F}$ driven by a generator with $V_0=80 \text{ V}$ and frequency 1200 Hz , find the voltages across the capacitor, resistor and the inductor at $t=0.1 \text{ s}$ after the generator is turned on at $t=0$.

Solution:

We start by applying the loop rule to the circuit as follows:

$$V_0 \sin \omega t - I.R - L \frac{dI}{dt} - \frac{Q}{C} = 0 \text{ where } Q \text{ is the charge on the capacitor.}$$

The solution to this equation may be taken as: $Q = -Q_0 \cos(\omega t - \mathbf{j})$

Where the phase angle $\mathbf{j} = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$ can be calculated to be 51.5° .

If we can find Q_0 then we have the charge Q completely given at any time and from this we can calculate the current $I=dQ/dt$ and hence the voltages across the individual components.

We can write $Q_0 = V_{\max} .C$ where V_{\max} is the maximum potential on the capacitor. This maximum is given by:

$$V_{\max} = V_0 \frac{X_C}{Z} = \frac{V_0}{\omega C Z} \text{ and hence } Q_0 = \frac{V_0}{Z \omega} \text{ where } Z \text{ is the total series impedance}$$

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

Thus: $Q = -\frac{V_0}{Z \omega} \cos(\omega t - \mathbf{j})$ and differentiating this gives $I(t) = \left(\frac{V_0}{Z} \right) \sin(\omega t - \mathbf{j})$

We can use the current to find the voltage across the inductor by:

$$V_L = L \frac{dI}{dt} = \frac{L V_0 \omega}{Z} \cos(\omega t - \mathbf{j}) = 43.0 \text{ V}$$

The voltage across the resistor is of course:

$$V_R = I.R = \frac{V_0 R}{Z} \sin(\omega t - \mathbf{j}) = -39.0 \text{ V}$$

The voltage across the capacitor is:

$$V_C = \frac{Q}{C} = -\frac{V_0}{Z C \omega} \cos(\omega t - \mathbf{j}) = -4.0 \text{ V}$$

Note that $V_L + V_R + V_C = 0$ since at $t = 0.1 \text{ s}$ one completes 120 cycles and the circuit is back to where it started at $t=0$ i.e. the generator voltage was zero.