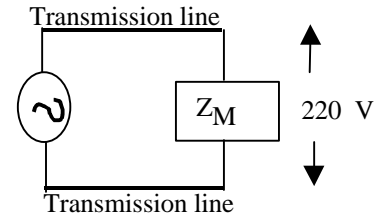


Prob3455: An electric motor consumes 5 kW of power at 220 V amplitude with a power factor of 0.80. This motor runs at the end of a transmission line of resistance 2.5 Ω. What voltage and power must be supplied at the input end of the transmission line.

Solution:

Let us first find the current through the motor - this given the resistance of the transmission line will give us the additional voltage needed.



The power in the motor

$$\langle P_M \rangle = \left(\frac{V_0^2}{2Z_M} \right) \cos \phi = 5 \text{ kW}$$

$$\text{Therefore } Z_M = \frac{V_0^2}{2 \langle P_M \rangle} \cos \phi = 3.87 \Omega$$

$$\text{Hence the peak current thru the motor is } I_0 = \frac{V_0}{Z_M} = 56.8 \text{ A}$$

In order to use this information to find the peak voltage needed from the generator we need to find the total impedance Z_T

Note: You cannot set $V_{0T} = I_0 \cdot Z_M + I_0 \cdot Z_T$. This is because in AC circuits impedances do not add linearly just like simple resistors. The reactive parts and the resistive parts of two series impedances must be treated separately according to the recipe

$$Z_T = \sqrt{[(X_{L1} + X_{L2}) - (X_{C1} + X_{C2})]^2 + (R_1 + R_2)^2}$$

In our case this means that:

$$Z_T = \sqrt{[X_{LM} - X_{CM}]^2 + (R_M + R_t)^2} \text{ since the reactive parts of the transmission line are zero.}$$

$$\text{Since } Z_M = \sqrt{[X_{LM} - X_{CM}]^2 + R_M^2} \text{ implies that } Z_M^2 - R_M^2 = [X_{LM} - X_{CM}]^2 \text{ we have}$$

$$Z_T = \sqrt{Z_M^2 - R_M^2 + (R_M + R_t)^2} = 6.07 \Omega \text{ (since } R_M = Z_M \cos \phi = 3.87 \times 0.8 = 3.1 \Omega \text{).}$$

Thus

$$V_{0T} = I_0 \cdot Z_T = 56.8 \times 6.1 = 345 \text{ V}$$

The power that needs to be supplied is:

$$\langle P_T \rangle = \left(\frac{V_{0T}^2}{2Z_T} \right) (R_t + R_M) = 9.05 \text{ kW}$$

Final Note: This is a lot harder way to do the problem than by using complex numbers !