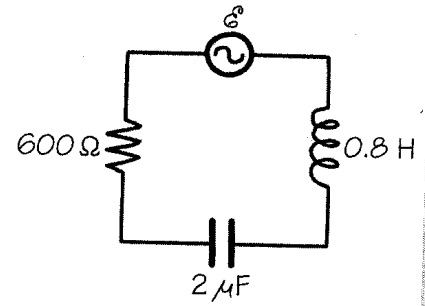


Prob34-33: Given that the maximum voltage in the circuit shown in the figure is 110 V and the frequency of oscillation is 60 Hz, calculate the maximum current and the maximum potential drops across the resistor, capacitor, and inductor.



What is the resonant angular frequency ω_0 of the circuit ?
 Suppose that the voltage generator has a variable angular frequency ω for what values of ω will the current have half the value it has at resonance?

Solution:

We know that $X_C = \frac{1}{\omega C} = 1.33 \text{ k}\Omega$

And $X_L = \omega L = 302 \Omega$. And therefore $Z = \sqrt{(X_L - X_C)^2 + R^2} = 1.2 \text{ k}\Omega$.

The maximum current in the circuit therefore is:

$$I_0 = \frac{V_0}{Z} = 110 \text{ V} / 1.2 \text{ k} = 92 \text{ mA}.$$

The potential differences therefore are:

$$V_{R0} = I_0 \cdot R = 55 \text{ V}$$

$$V_{C0} = I_0 \cdot \frac{1}{\omega C} = 123 \text{ V}$$

and

$$V_{L0} = I_0 \cdot \omega L = 28.0 \text{ V}$$

The answer for the last part : the required frequency is $1.7 \times 10^3 \text{ rad/s}$.