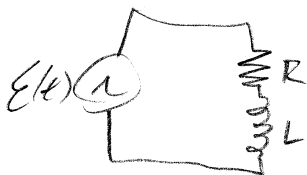


## Homework #10

Tipler 28-62, 66, 75, 2 others

28-62



$$E_{\text{rms}} = 120 \text{ V}$$

$$\omega = 2\pi \cdot 60 \text{ Hz}$$

$$P_{\text{ave}} = 60 \text{ W}$$


$$I_{\text{rms}} = 1.5 \text{ A}$$

$$a) \text{ Power factor} = \cos \delta = \frac{P_{\text{av}}}{E_{\text{rms}} I_{\text{rms}}} = \frac{1}{3}$$

$$b) I_{\text{rms}} Z_T = E_{\text{rms}} \quad Z_T = \frac{E_{\text{rms}}}{I_{\text{rms}}} = \frac{120}{1.5} = 80 \Omega$$

$$R = Z_T \cos \delta = 80 \Omega \cdot \frac{1}{3} \approx 26.7 \Omega$$
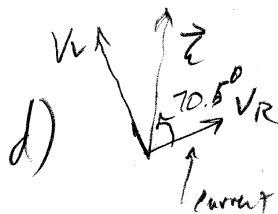
$$c) Z_T^2 = R^2 + \omega^2 L^2 \Rightarrow L^2 = \frac{Z_T^2 - R^2}{\omega^2} = \frac{80^2 (1 - \frac{1}{9})}{(2\pi)^2 (60)^2}$$



$$L = 0.2 \text{ H}$$

Current lags voltage

$$\delta = \cos^{-1} \frac{1}{3} = 70.5^\circ$$

28.66





$X_C = 10 \Omega$   
 $X_L = 30 \Omega$   
 $R_1 = 10 \Omega$   
 $R_2 = 40 \Omega$

a)  $Z_1 = \sqrt{R_1^2 + X_C^2} = \sqrt{10^2 + 10^2} = 10\sqrt{2} \Omega = 14.14 \Omega$   
 $Z_2 = \sqrt{R_2^2 + X_L^2} = \sqrt{40^2 + 30^2} = 50 \Omega$

b)  $I_1 = \frac{E}{Z_1} = \frac{E}{14.14 \Omega}$      $\cos \delta_1 = \frac{R_1}{Z_1} = \frac{10}{14.14} = \frac{1}{\sqrt{2}}$      $\delta_1 = 45^\circ$  lead V  
 $I_2 = \frac{E}{Z_2} = \frac{E}{50 \Omega}$      $\cos \delta_2 = \frac{R_2}{Z_2} = \frac{40}{50} \Rightarrow \delta_2 = \cos^{-1} \frac{40}{50} = 36.87^\circ$  lag V

c)

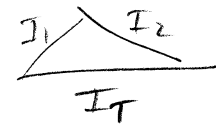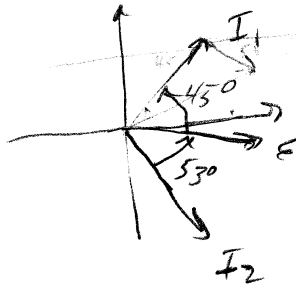

$\vec{I}_T = \vec{I}_1 + \vec{I}_2$   
 $= I_1 \left( \frac{1}{\sqrt{2}} \hat{i} + \frac{1}{\sqrt{2}} \hat{j} \right) + I_2 \left( \cos \delta_2 \hat{i} - \sin \delta_2 \hat{j} \right)$   
 $= \left( \frac{I_1}{\sqrt{2}} + I_2 \cos \delta_2 \right) \hat{i} + \left( \frac{I_1}{\sqrt{2}} - I_2 \sin \delta_2 \right) \hat{j}$

$|I_T| = \frac{E}{13.131}$




$\delta_2 = 36.87^\circ$

$\frac{\sin \delta}{\frac{1}{\sqrt{2}}} = \frac{\sin(180^\circ - 45^\circ - 36.87^\circ)}{\frac{1}{\sqrt{2}}}$

phase angle =  $45^\circ - \delta = 29.9^\circ$

$\delta = 13.06^\circ$

28.75.

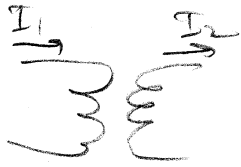

$$P = I_1 E_1 = I_2 E_2$$

$$\frac{E_2}{N_2} = \frac{E_1}{N_1}$$


$$N_1 I_1 = N_2 I_2$$

$$I_1 = I_2 \frac{E_2}{E_1}$$

$$= \frac{E_2}{Z} \cdot \frac{E_2}{E_1} = \frac{E_1^2 \cdot \left(\frac{N_2}{N_1}\right)^2}{Z E_1} = \frac{E_1}{\left(\frac{N_1}{N_2}\right)^2 Z}$$

$$\Rightarrow Z_{\text{eff}} = \left(\frac{N_1}{N_2}\right)^2 Z$$

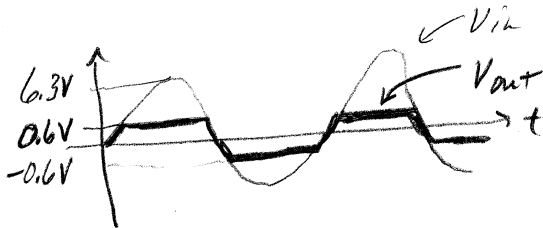4. The diodes limit the output to a diode drop  $0.6V$ , neglecting other diode effects. The transformer is just an AC source, and the resistor is just to limit current. So we have



5. The current gain is  $\beta = \frac{I_{\text{collector}}}{I_{\text{base}}} = \frac{0.5 \text{ mA}}{10 \mu\text{A}} = 50.$

So the voltage gain is  $\frac{V_L}{V_S} = \beta \cdot \frac{R_L}{R_B} = 50 \cdot \frac{10 \text{ k}\Omega}{2 \text{ k}\Omega} = 250.$