

## **ConceptTest 26.3b**

## **Wires II**

A wire of resistance  $R$  is stretched uniformly (keeping its volume constant) until it is twice its original length. What happens to the resistance?

- 1) it decreases by a factor 4
- 2) it decreases by a factor 2
- 3) it stays the same
- 4) it increases by a factor 2
- 5) it increases by a factor 4

## ConceptTest 26.3b

## Wires II

A wire of resistance  $R$  is stretched uniformly (keeping its volume constant) until it is twice its original length. What happens to the resistance?

- 1) it decreases by a factor 4
- 2) it decreases by a factor 2
- 3) it stays the same
- 4) it increases by a factor 2
- 5) it increases by a factor 4

Keeping the volume (= area x length) constant means that if the length is **doubled**, the area is **halved**.


Since  $R = \rho \frac{L}{A}$ , this increases the resistance by **four**.

## ConceptTest 26.4a

## Series Resistors I

Assume that the voltage of the battery is **9 V** and that the three resistors are **identical**.  
What is the potential difference across each resistor?

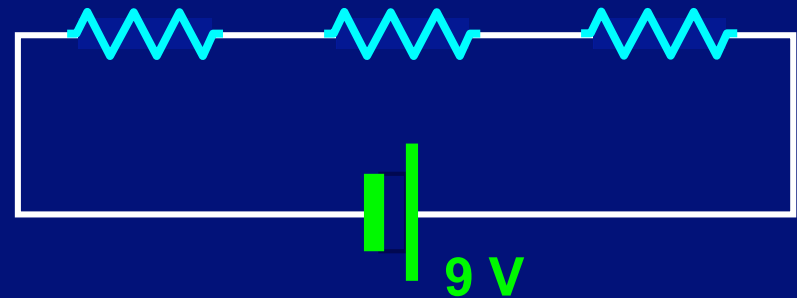- 1) 12 V
- 2) zero
- 3) 3 V
- 4) 4 V
- 5) you need to know the actual value of  $R$



## ConceptTest 26.4a

## Series Resistors I

Assume that the voltage of the battery is **9 V** and that the three resistors are **identical**. What is the potential difference across each resistor?

1) 12 V


2) zero

3) 3 V

4) 4 V

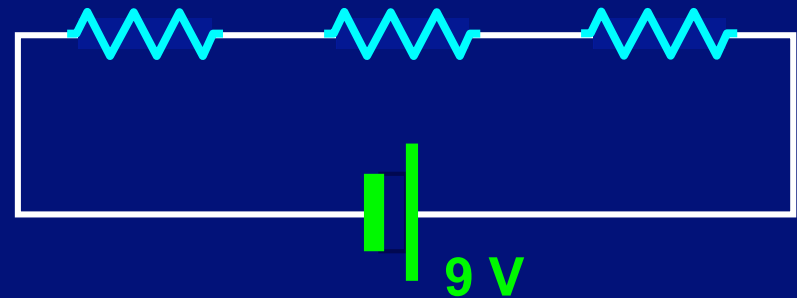5) you need to know the actual value of  $R$

Since the resistors are all **equal**, the voltage will drop **evenly** across the 3 resistors, with  $1/3$  of 9 V across each one. So we get a **3 V** drop across each.




**Follow-up:** What would be the potential difference if  $R = 1\ \Omega, 2\ \Omega, 3\ \Omega$

## ConceptTest 26.6b

## Short Circuit II

Two lightbulbs A and B are connected in series to a constant voltage source. When a wire is connected across B, bulb A will:

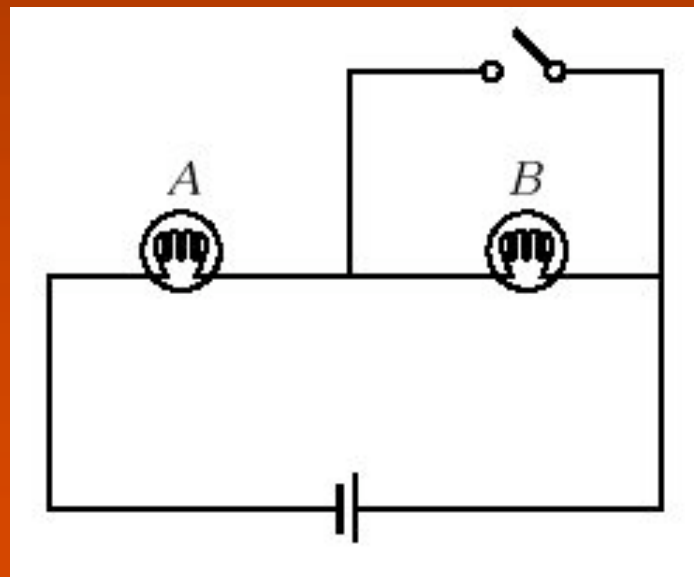- 1) glow brighter than before
- 2) glow just the same as before
- 3) glow dimmer than before
- 4) go out completely
- 5) explode




## ConceptTest 26.6b

## Short Circuit II

Two lightbulbs A and B are connected in series to a constant voltage source. When a wire is connected across B, bulb A will:

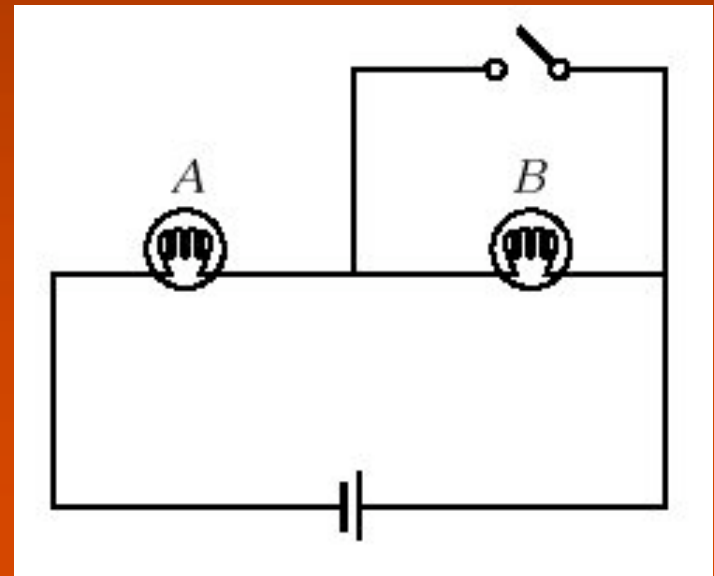- 1) glow brighter than before
- 2) glow just the same as before
- 3) glow dimmer than before
- 4) go out completely
- 5) explode

Since bulb B is bypassed by the wire, the total resistance of the circuit decreases. This means that the current through bulb A increases.




Follow-up: What happens to bulb B?

## ConceptTest 26.8a

## More Circuits I

What happens to the voltage across the resistor  $R_1$  when the switch is closed? The voltage will:

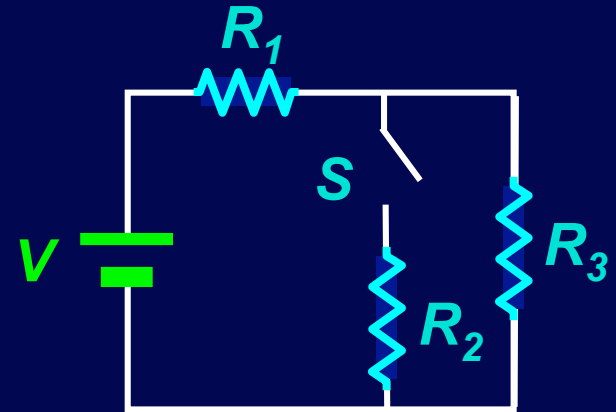- 1) increase
- 2) decrease
- 3) stay the same




## ConceptTest 26.8a

## More Circuits I

What happens to the voltage across the resistor  $R_1$  when the switch is closed? The voltage will:

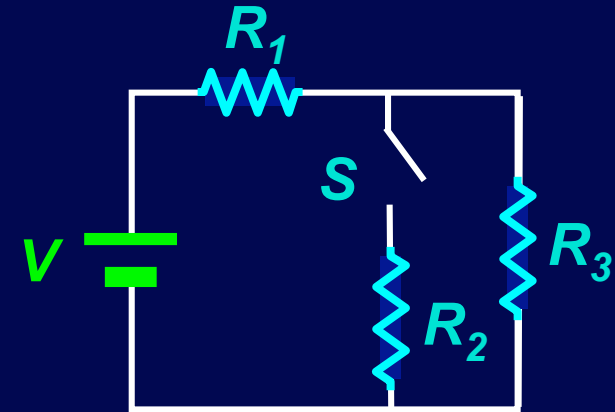- 1) increase
- 2) decrease
- 3) stay the same

With the switch closed, the addition of  $R_2$  to  $R_3$  decreases the equivalent resistance, so the current from the battery increases. This will cause an increase in the voltage across  $R_1$ .



**Follow-up:** What happens to the current through  $R_3$ ?