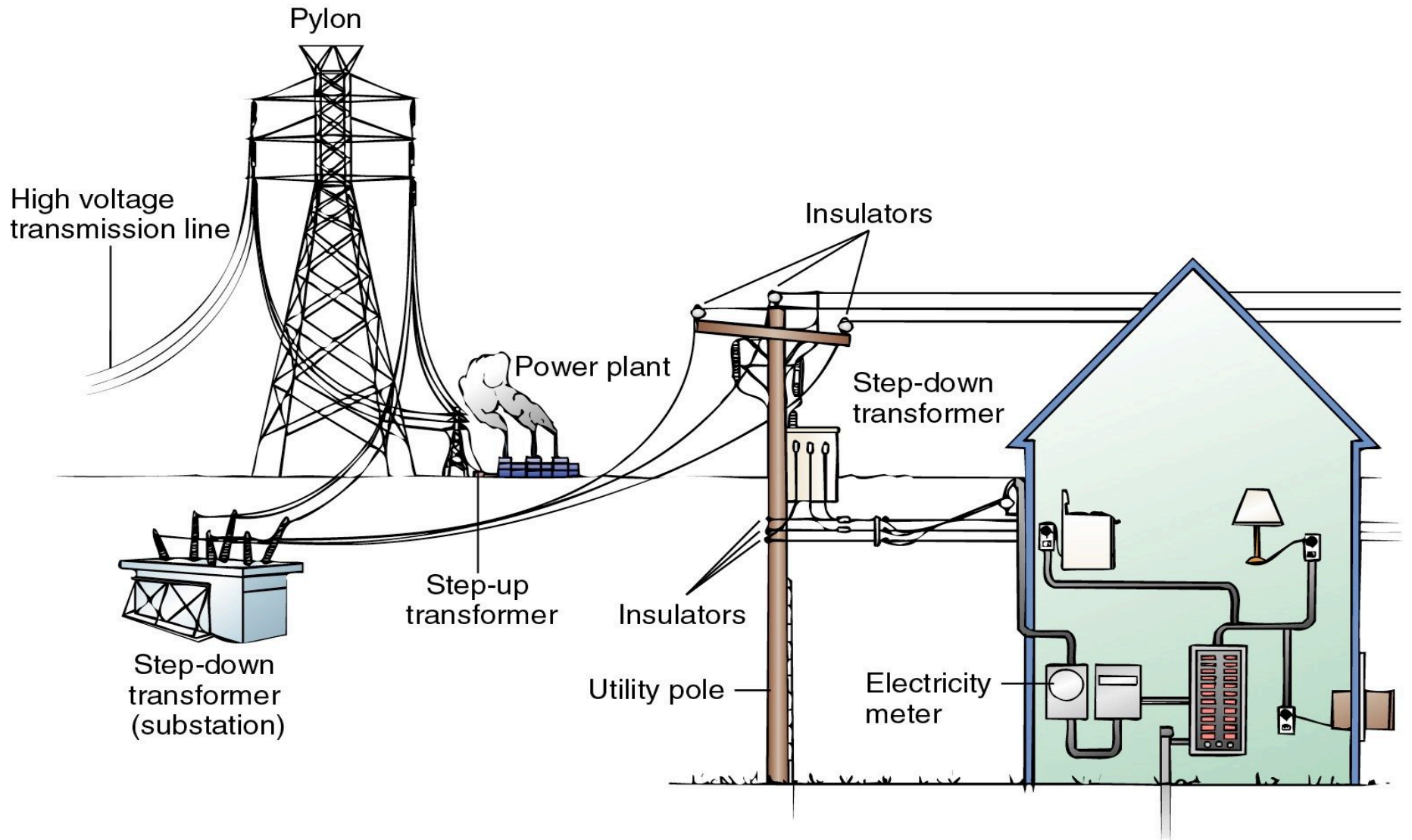


# Lecture 7 Circuits Ch. 27


- Cartoon -Kirchhoff's Laws
- Warm-up problems
- Topics
  - Direct Current Circuits
  - Kirchhoff's Two Rules
  - Analysis of Circuits Examples
  - Ammeter and voltmeter
  - RC circuits
- Demos
  - Three bulbs in a circuit
  - Power loss in transmission lines
  - Resistivity of a pencil
  - Blowing a fuse

# Transmission line demo




## Direct Current Circuits

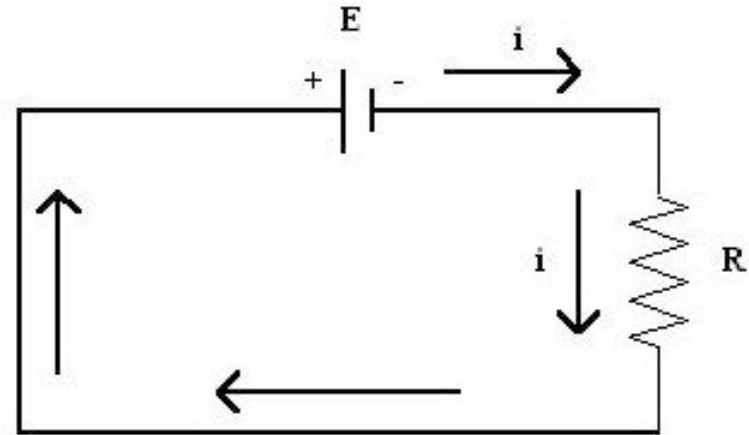1. The sum of the potential drops around a closed loop is zero. This follows from energy conservation and the fact that the electric field is a conservative force.



$$E - iR = 0$$

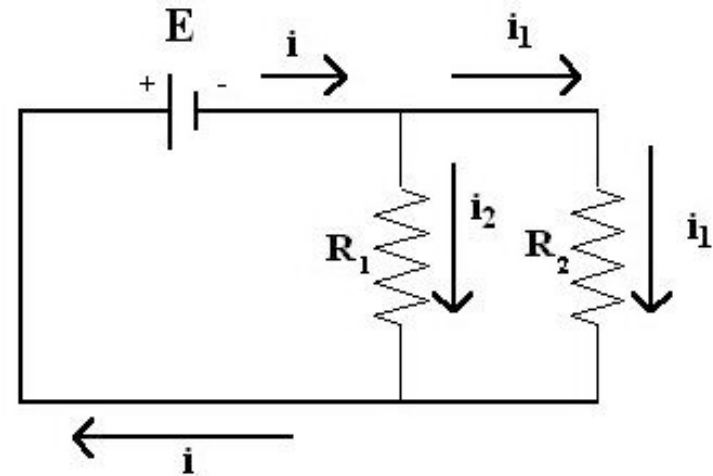2. The sum of currents into any junction of a closed circuit must equal the sum of currents out of the junction. This follows from charge conservation.



$$i = i_1 + i_2$$

## Example (Single Loop Circuit)

No junction so we don't need that rule.

How do we apply Kirchoff's rule?

Must assume the direction of the current –  
assume clockwise.



Choose a starting point and apply Ohm's Law as  
you go around the circuit.

- a. Potential across resistors is negative
- b. Sign of E for a battery depends on assumed current flow
- c. If you guessed wrong on the sign, your answer will be negative

Start in the upper left hand corner.

$$-iR_1 - iR_2 - E_2 - ir_2 - iR_3 + E_1 - ir_1 = 0$$
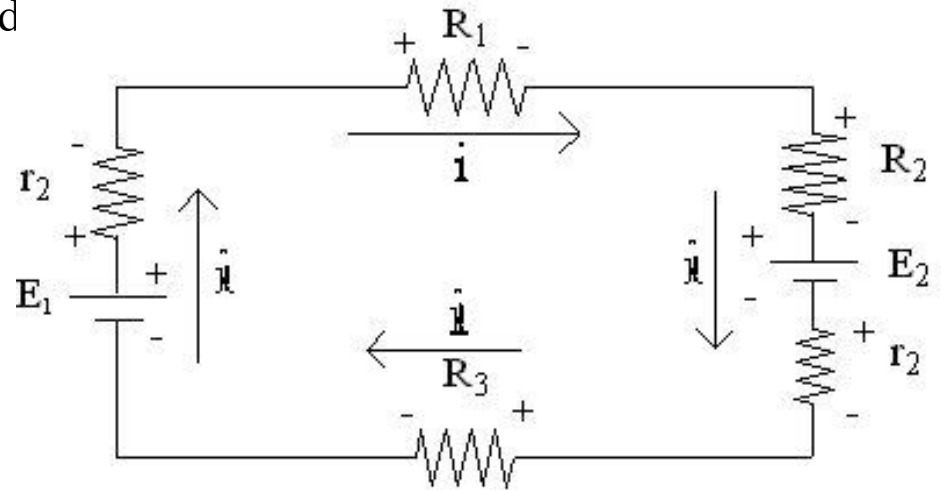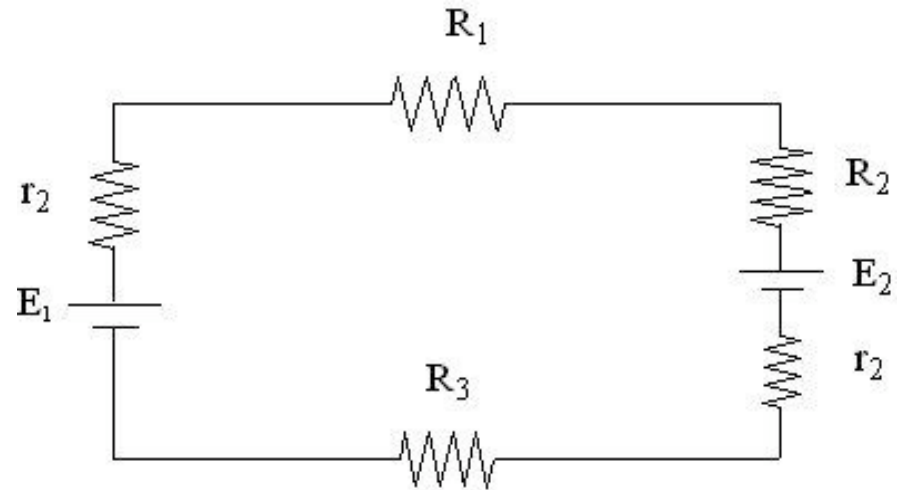
$$i = \frac{E_1 - E_2}{R_1 + R_2 + R_3 + r_1 + r_2}$$



$$i = \frac{E_1 - E_2}{R_1 + R_2 + R_3 + r_1 + r_2}$$

Now let us put in numbers.

Suppose:  $R_1 = R_2 = R_3 = 10\Omega$

$$r_1 = r_2 = 1\Omega$$

$$E_1 = 10V$$

$$E_2 = 5V$$

$$i = \frac{10 - 5}{10 + 10 + 10 + 1 + 1} \frac{V}{\Omega} = \frac{5}{32} \text{ amp}$$

Suppose:  $E_1 = 5V$

$$E_2 = 10V$$

$$i = \frac{(5 - 10)V}{32\Omega} = \frac{-5}{32} \text{ amp}$$

We get a minus sign. It means our assumed direction of current must be reversed.

Note that we could have simply added all resistors and get the  $R_{eq.}$  and added the EMFs to get the  $E_{eq.}$  And simply divided.

$$i = \frac{E_{eq.}}{R_{eq.}} = \frac{5(V)}{32(\Omega)} = \frac{5}{32} \text{ amp}$$

### Sign of EMF


Battery **1** current flows from - **to** + in battery **+E<sub>1</sub>**

Battery **2** current flows from + **to** - in battery **-E<sub>2</sub>**

In **1** the electrical potential energy **increases**

In **2** the electrical potential energy **decreases**

## Example with numbers

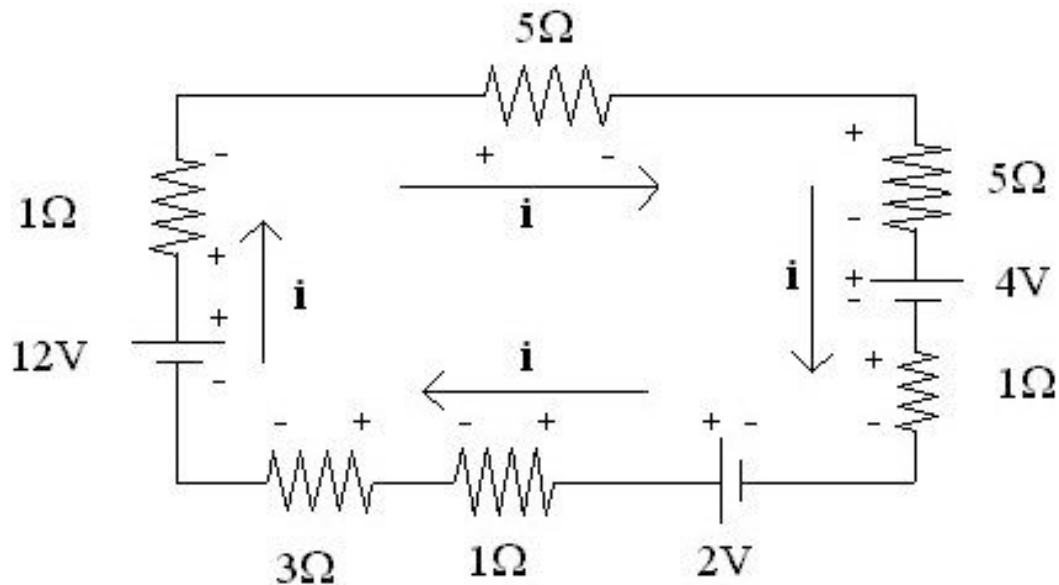

Quick solution:

$$\sum_{i=1}^3 E_i = 12V - 4V + 2V = 10V$$

$$\sum_{i=1}^6 R_i = 16\Omega$$

$$I = \frac{E_{eq.}}{R_{eq.}} = \frac{10}{16} A$$

**Question: What is the current in the circuit?**

Write down Kirchoff's loop equation.

Loop equation


Assume current flow is clockwise.

Do the batteries first – Then the current.

$$(+12 - 4 + 2)V - i(1 + 5 + 5 + 1 + 1 + 3)\Omega = 0$$

$$i = \frac{10 V}{16 \Omega} = 0.625 \text{ amps} = 0.625 A$$

## Example with numbers (continued)

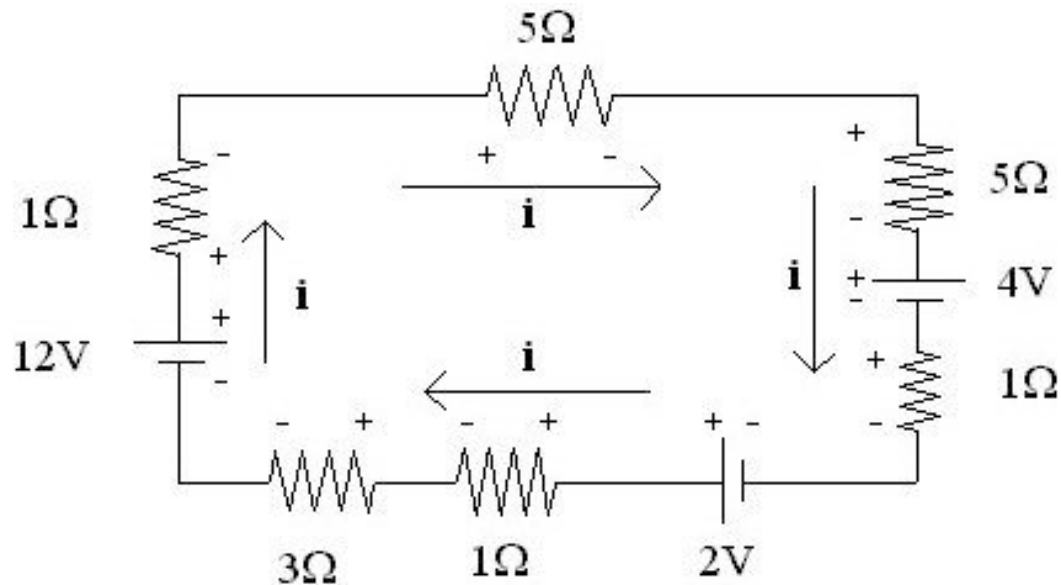


**Question: What are the terminal voltages of each battery?**

$$12\text{V: } V = \mathcal{E} - ir = 12\text{V} - 0.625\text{A} \cdot 1\Omega = 11.375\text{V}$$

$$2\text{V: } V = \mathcal{E} - ir = 2\text{V} - 0.625\text{A} \cdot 1\Omega = 1.375\text{V}$$

$$4\text{V: } V = \mathcal{E} - ir = 4\text{V} + 0.625\text{A} \cdot 1\Omega = 4.625\text{V}$$

# Multiloop Circuits

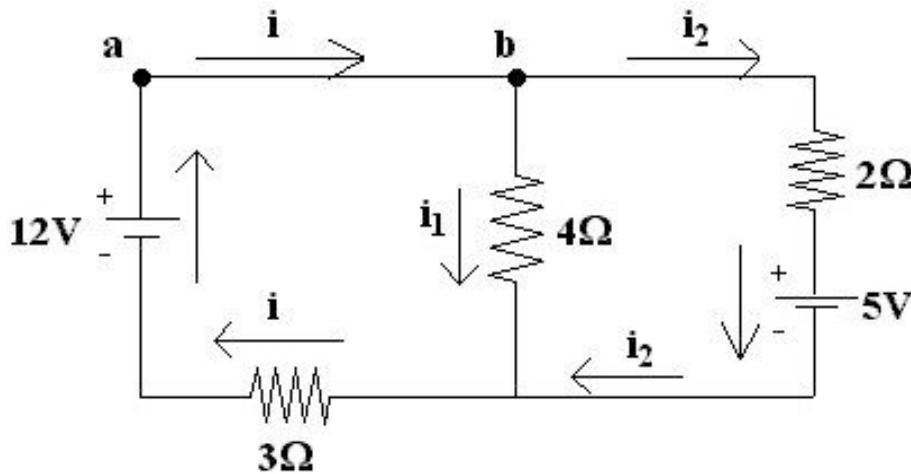

Find  $i$ ,  $i_1$ , and  $i_2$

We now have 3 equations with 3 unknowns.

$$12 - 4i_1 - 3(i_1 + i_2) = 0$$

$$12 - 7i_1 - 3i_2 = 0 \quad \text{multiply by 2}$$

$$-5 + 4i_1 - 2i_2 = 0 \quad \text{multiply by 3}$$

$$24 - 14i_1 - 6i_2 = 0$$

$$-15 + 12i_1 - 6i_2 = 0 \quad \text{subtract them}$$

$$39 - 26i_1 = 0$$

$$i_1 = \frac{39}{26} = 1.5A$$

$$i_2 = 0.5A$$

$$i = 2.0A$$

Find the Joule heating in each resistor  $P=i^2R$ .

Is the 5V battery being charged?

## Kirchoff's Rules

1.  $\sum_i V_i = 0$  in any loop

2.  $\sum i_{in} = \sum i_{out}$  at any junction

Rule 1 – Apply to 2 loops (2 inner loops)

a.  $12 - 4i_1 - 3i = 0$

b.  $-2i_2 - 5 + 4i_1 = 0$

Rule 2

a.  $i = i_1 + i_2$



## Method of determinants for solving simultaneous equations

$$\begin{aligned}i - i_1 - i_2 &= 0 \\ -3i - 4i_1 + 0 &= -12 \\ 0 + 4i_1 - 2i_2 &= 5\end{aligned}$$

Cramer's Rule says if :

$$\begin{aligned}a_1i_1 + b_1i_2 + c_1i_3 &= d_1 \\ a_2i_1 + b_2i_2 + c_2i_3 &= d_2 \\ a_3i_1 + b_3i_2 + c_3i_3 &= d_3\end{aligned}$$

Then,

$$i_1 = \frac{\begin{vmatrix} d_1 & b_1 & c_1 \\ d_2 & b_2 & c_2 \\ d_3 & b_3 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix}}$$

$$i_2 = \frac{\begin{vmatrix} a_1 & d_1 & c_1 \\ a_2 & d_2 & c_2 \\ a_3 & d_3 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix}}$$

$$i_3 = \frac{\begin{vmatrix} a_1 & b_1 & d_1 \\ a_2 & b_2 & d_2 \\ a_3 & b_3 & d_3 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix}}$$

Method of determinants using Cramers Rule and cofactors  
 Also use this to remember how to evaluate cross products  
 of two vectors.

For example solve for  $i$


$$i = \frac{\begin{vmatrix} 0 & -1 & -1 \\ -12 & -4 & 0 \\ 5 & +4 & -2 \end{vmatrix}}{\begin{vmatrix} 1 & -1 & -1 \\ -3 & -4 & 0 \\ 0 & +4 & -2 \end{vmatrix}} = \frac{0 \begin{pmatrix} -4 & 0 \\ 4 & -2 \end{pmatrix} - 1 \begin{pmatrix} 0 & -12 \\ -2 & 5 \end{pmatrix} - 1 \begin{pmatrix} -12 & -4 \\ 5 & 4 \end{pmatrix}}{1 \begin{pmatrix} -4 & 0 \\ 4 & -2 \end{pmatrix} - 1 \begin{pmatrix} 0 & -3 \\ -2 & 0 \end{pmatrix} - 1 \begin{pmatrix} -3 & -4 \\ 0 & 4 \end{pmatrix}} = \frac{24 + 48 - 20}{8 + 6 + 12} = \frac{52}{26} = 2A$$

You try it for  $i_1$  and  $i_2$ .

See inside of front cover in your book on how to use Cramer's Rule.

## Another example

Find all the currents including directions.

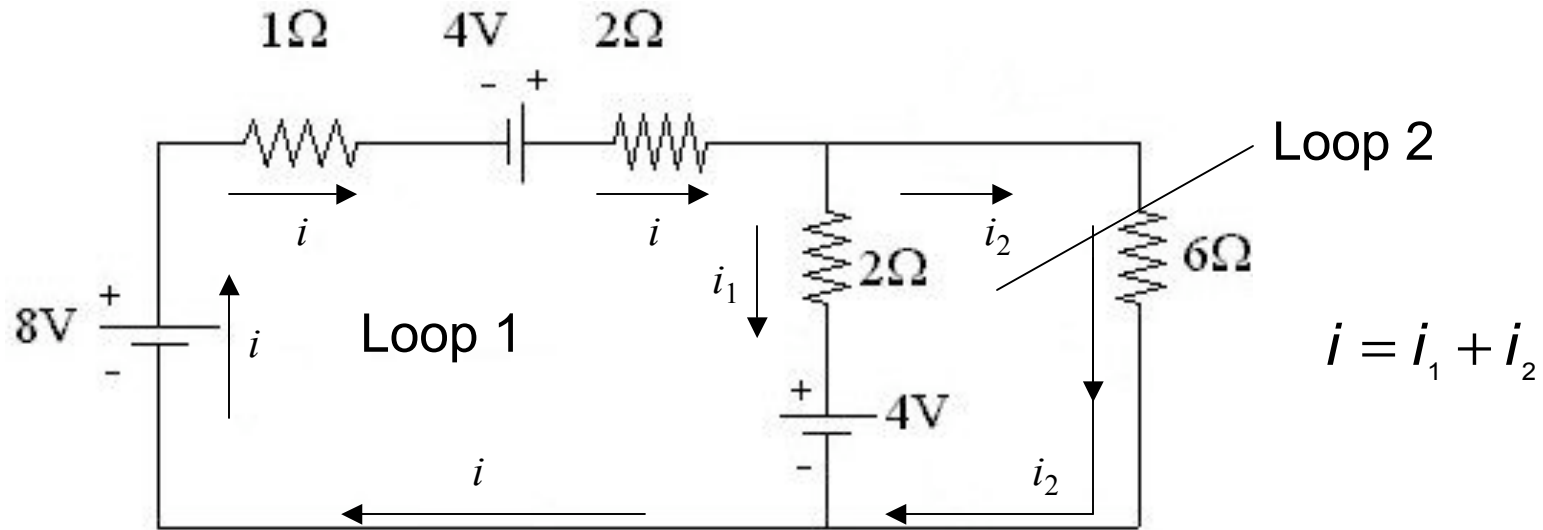

Loop 1

$$0 = +8V + 4V - 4V - 3i - 2i_1$$

$$0 = 8 - 3i_1 - 3i_2 - 2i_1$$

$$0 = 8 - 5i_1 - 3i_2$$

Loop 2

$$-6i_2 + 4 + 2i_1 = 0$$

Multiply eqn of loop 1 by 2 and subtract from the eqn of loop 2

$$-6i_2 + 4 + 2i_1 = 0$$

$$-6i_2 + 16 - 10i_1 = 0$$

$$\hline 0 - 12 + 12i_1 = 0$$

$$\boxed{i_1 = 1A}$$


$$-6i_2 + 4 + 2(1A) = 0$$

$$\boxed{i_2 = 1A}$$

$$\boxed{i = 2A}$$

## Rules for solving multiloop circuits

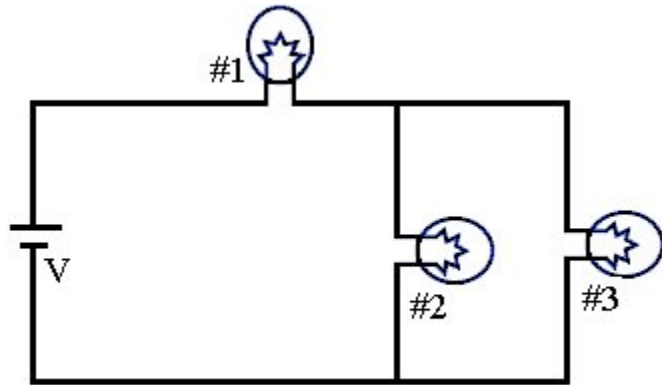1. Replace series resistors or batteries with their equivalent values.
2. Choose a direction for  $i$  in each loop and label diagram.
3. Write the junction rule equation for each junction.
4. Apply the loop rule  $n$  times for  $n$  interior loops.
5. Solve the equations for the unknowns. Use Cramer's Rule if necessary.
6. Check your results by evaluating potential differences.




## 3 bulb question

The circuit above shows three identical light bulbs attached to an ideal battery. If the bulb#2 burns out, which of the following will occur?

- a) Bulbs 1 and 3 are unaffected. The total light emitted by the circuit decreases.
- b) Bulbs 1 and 3 get brighter. The total light emitted by the circuit is unchanged.
- c) Bulbs 1 and 3 get dimmer. The total light emitted by the circuit decreases.
- d) Bulb 1 gets dimmer, but bulb 3 gets brighter. The total light emitted by the circuit is unchanged.
- e) Bulb 1 gets brighter, but bulb 3 gets dimmer. The total light emitted by the circuit is unchanged.
- f) Bulb 1 gets dimmer, but bulb 3 gets brighter. The total light emitted by the circuit decreases.
- g) Bulb 1 gets brighter, but bulb 3 gets dimmer. The total light emitted by the circuit decreases.
- h) Bulb 1 is unaffected, but bulb 3 gets brighter. The total light emitted by the circuit increases.
- i) None of the above.

When the bulb #2 is not burnt out:

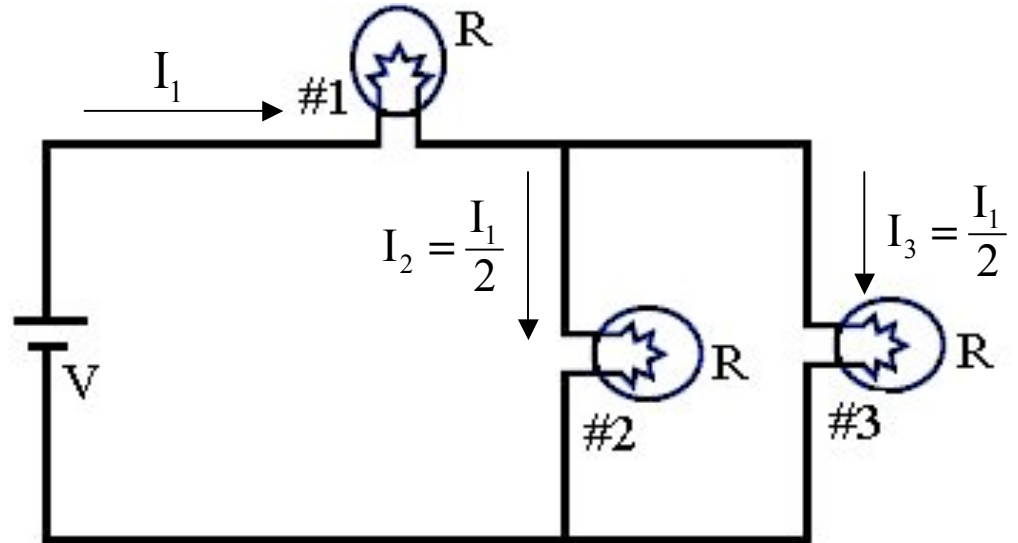

$$R_{\text{eq}} = R + \frac{R}{2} = \frac{3}{2}R$$

$$\text{Power, } P = I^2R \quad I = \frac{V}{R}$$

For Bulb #1

$$I_1 = \frac{V}{\frac{3}{2}R} = \frac{2V}{3R} \quad P_1 = I_1^2R = \frac{4V^2}{9R} = .44 \frac{V^2}{R}$$


For Bulb #2

$$I_2 = \frac{I_1}{2} = \frac{V}{3R} \quad P_2 = I_2^2R = \frac{V^2}{9R} = .11 \frac{V^2}{R}$$

For Bulb #3

$$I_3 = \frac{I_1}{2} = \frac{V}{3R} \quad P_3 = I_3^2R = \frac{V^2}{9R} = .11 \frac{V^2}{R}$$

When the bulb #2 is burnt out:

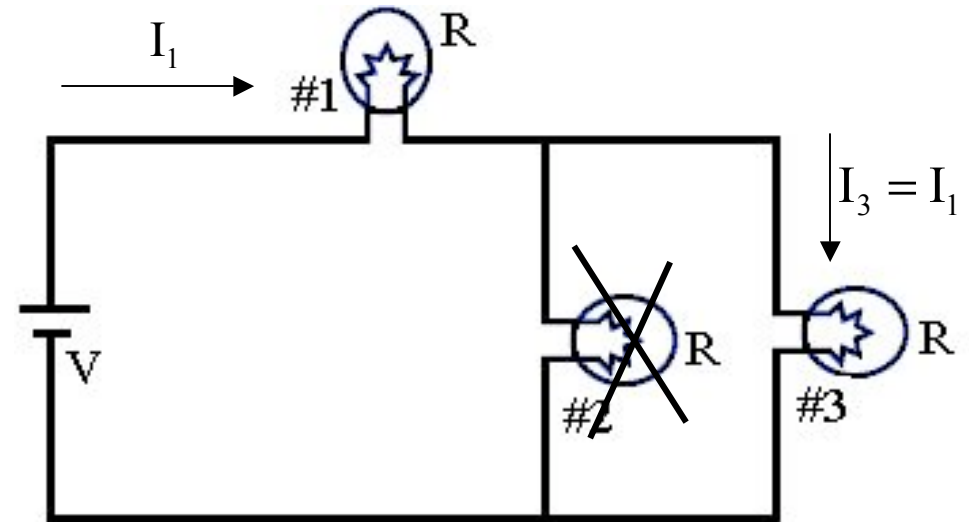

$$R_{eq} = R + R = 2R$$

$$\text{Power, } P = I^2 R \quad I = \frac{V}{R}$$

For Bulb #1

$$I_1 = \frac{V}{2R} \quad P_1 = I_1^2 R = \frac{V^2}{4R} = .25 \frac{V^2}{R}$$

For Bulb #2

$$I_2 = 0 \quad P_2 = I_2^2 R = 0$$

For Bulb #3

$$I_3 = I_1 = \frac{V}{2R} \quad P_3 = I_3^2 R = \frac{V^2}{4R} = .25 \frac{V^2}{R}$$


$$\text{Before total power was } P_b = \frac{V^2}{R_{eq}} = \frac{V^2}{\frac{3}{2}R} = .66 \frac{V^2}{R}$$

$$\text{After total power is } P_a = \frac{V^2}{R_{eq}} = \frac{V^2}{2R} = .50 \frac{V^2}{R}$$

So, Bulb #1 gets dimmer and bulb #3 gets brighter. And the total power decreases.

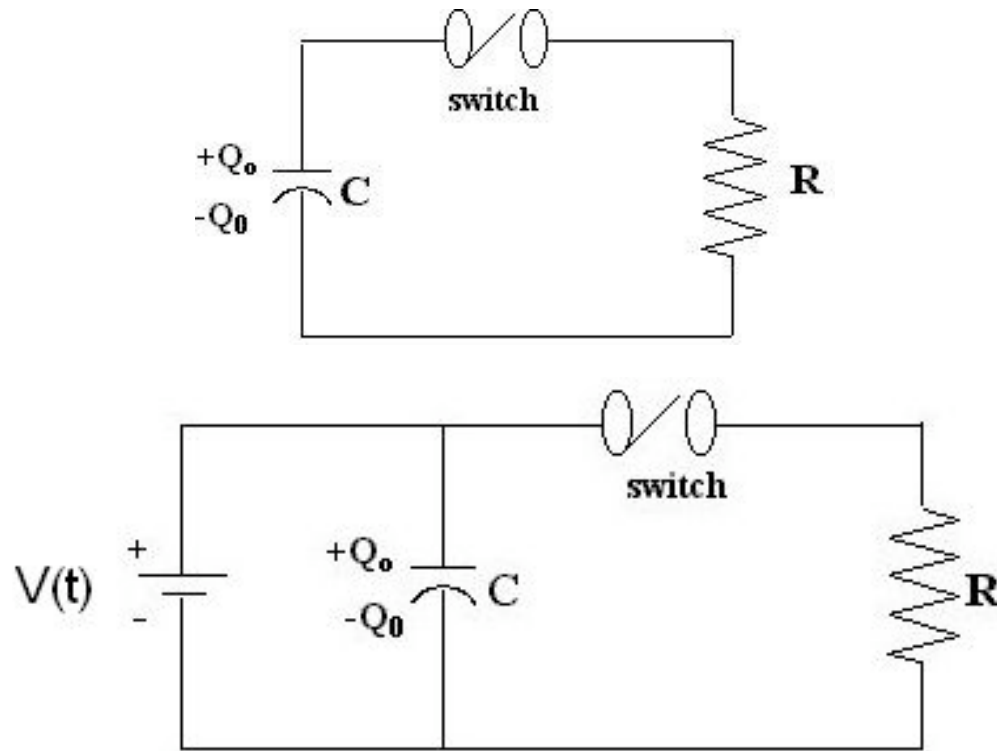f) is the answer.

How does a capacitor behave in a circuit with a resistor?



Charge capacitor with 9V battery with switch open, then remove battery.

Now close the switch. What happens?




# Discharging a capacitor through a resistor

Potential across capacitor =  $V = \frac{Q_o}{C}$   
just before you throw switch at time  $t = 0$ .

Potential across Resistor =  $iR$
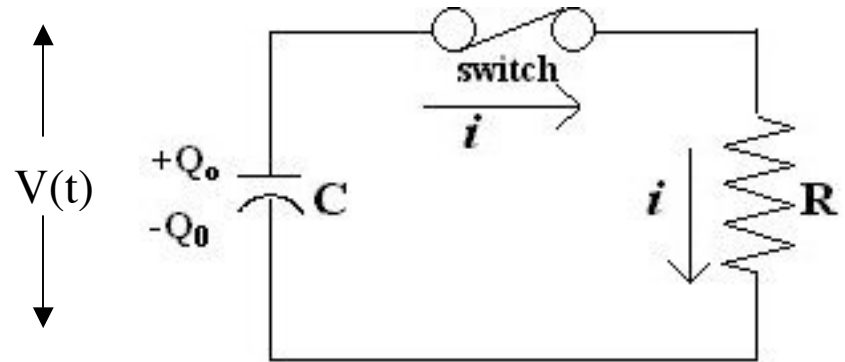
$$\frac{Q_o}{C} = i_o R \Rightarrow i_o = \frac{Q_o}{RC} \quad \text{at } t > 0.$$



What is the current  $I$  at time  $t$ ?

$$i(t) = \frac{Q(t)}{RC}$$

$$\text{or } i = \frac{Q}{RC}$$

# What is the current I at time t?

$$\text{So, } i = \frac{Q}{RC}, \quad \text{but } i = -\frac{dQ}{dt}$$

$$-\frac{dQ}{dt} = \frac{Q}{RC}$$

$$-\frac{dQ}{Q} = \frac{dt}{RC}$$

Time constant = RC

Integrating both the sides

$$-\int \frac{dQ}{Q} = \int \frac{dt}{RC}$$


$$-\ln Q = \frac{t}{RC} + A$$

$$\ln Q = -\frac{t}{RC} - A$$

$$\text{So, } Q = e^{-\frac{t}{RC} - A} = e^{-\frac{t}{RC}} e^{-A}$$

$$\text{At } t=0, Q=Q_0$$
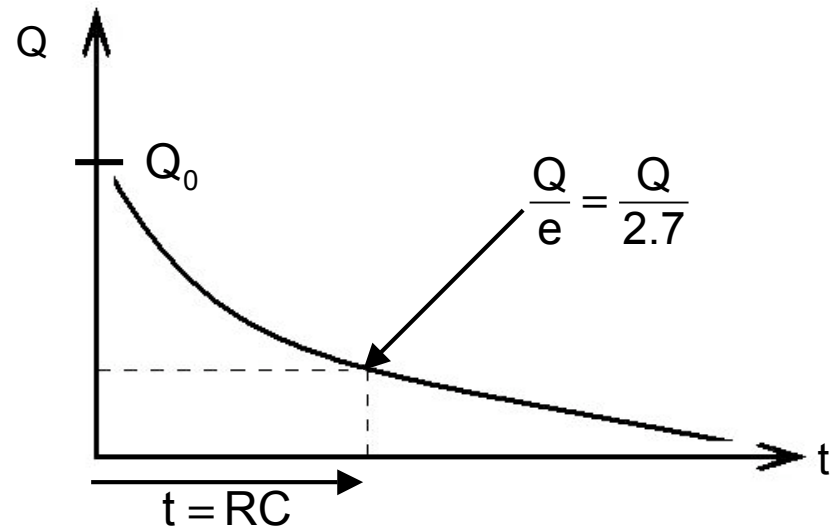
$$\text{So, } Q_0 = e^{-\frac{0}{RC} - A} = e^{-A}$$




$$\Rightarrow \boxed{Q = Q_0 e^{-\frac{t}{RC}}}$$

What is the current?


$$Q = Q_0 e^{-\frac{t}{RC}}$$
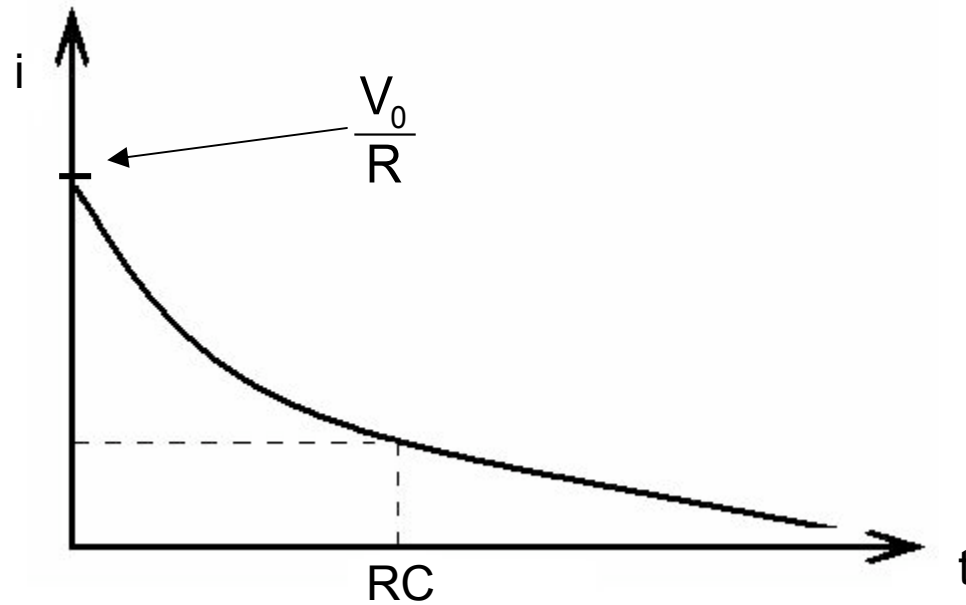
$$i = \frac{dQ}{dt} = -\frac{Q_0}{RC} e^{-\frac{t}{RC}} = -\frac{V_0}{R} e^{-\frac{t}{RC}} \quad \text{Ignore - sign}$$



# How the charge on a capacitor varies with time as it is being charged



What about charging the capacitor?

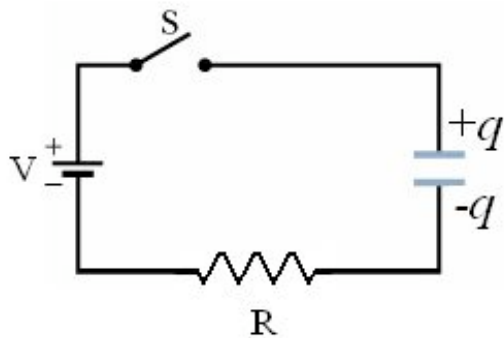

$$Q = CV_0(1 - e^{-\frac{t}{RC}})$$

$$i = \frac{V_0}{R} e^{-\frac{t}{RC}}$$

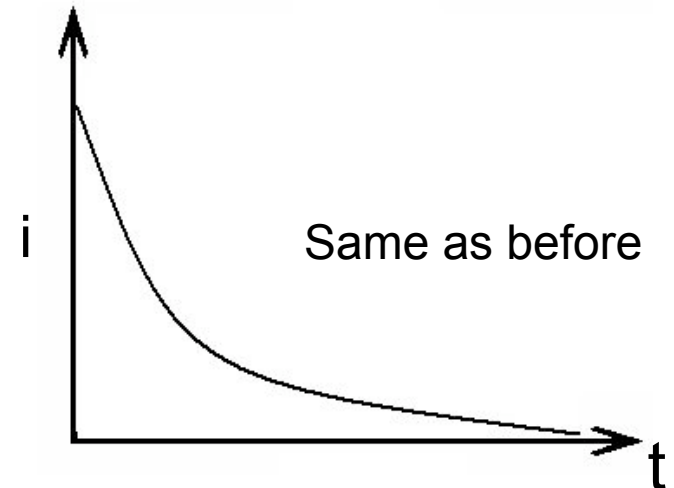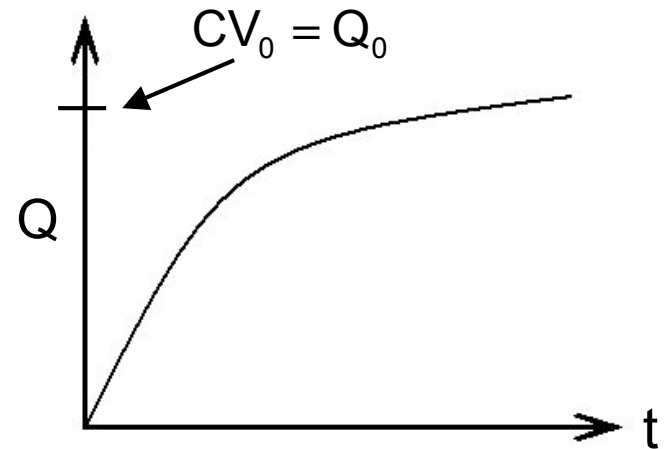Note that the current is zero when either the capacitor is fully charged or uncharged. But the second you start to charge it or discharge it, the current is maximum.




# Instruments

Galvanometers:	a coil in a magnetic field that senses current.
Ammeters:	measures current.
Voltmeter:	measures voltage.
Ohmmeters:	measures resistance.
Multimeters:	one device that does all the above.

Galvanometer is a needle mounted to a coil that rotates in a magnetic field.

The amount of rotation is proportional to the current that flows through the coil.


Symbolically we write

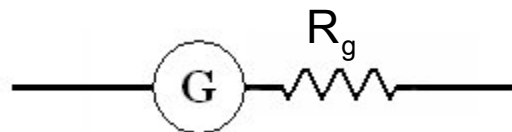

Usually when  $R_g = 20\Omega$

$I_g = 0 \rightarrow 0.5\text{milliAmp}$



# Ohmmeter

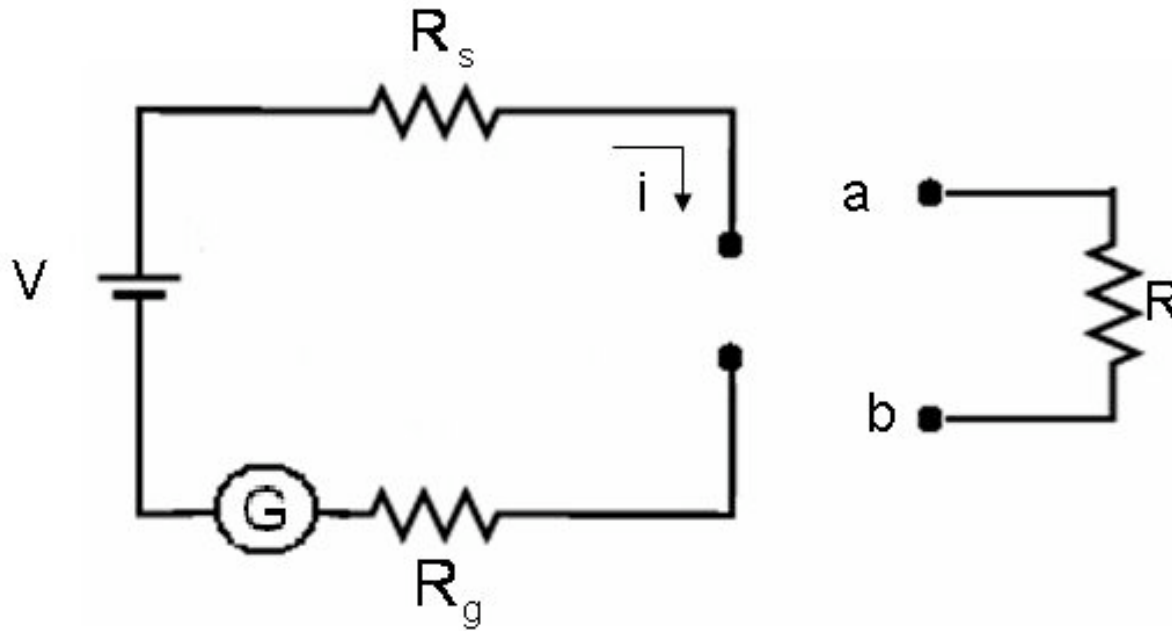

$$i = \frac{V}{R + R_s + R_g}$$

Adjust  $R_s$  so when  $R=0$  the galvanometer read full scale.

# Ammeter

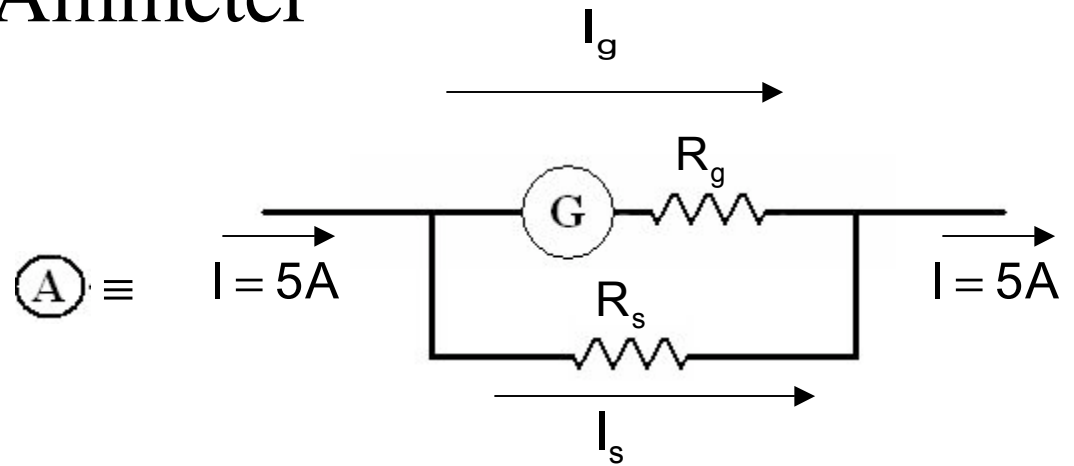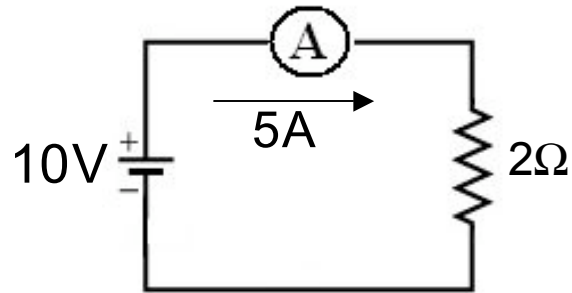

$$I = I_g + I_s = 5A$$

$$I_g R_g = I_s R_s$$

The idea is to find the value of  $R_s$  that will give a full scale reading in the galvanometer for 5A

$$R_g = 20\Omega \quad \text{and} \quad I_g = 0.5 \times 10^{-3} A, \quad \text{So,} \quad I_s = 5A - .0005A \approx 5A$$

$$\text{So,} \quad R_s = \frac{I_g}{I_s} R_g = \frac{0.5 \times 10^{-3} A}{5A} (20\Omega) = 0.002\Omega$$


Very small

Ammeters have very low resistance when put in series in a circuit.


You need a very stable shunt resistor.
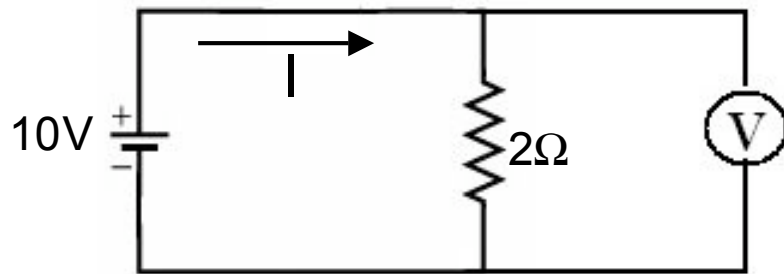
# Voltmeter

Use the same galvanometer to construct a voltmeter for which full scale reading in 10 Volts.



≡

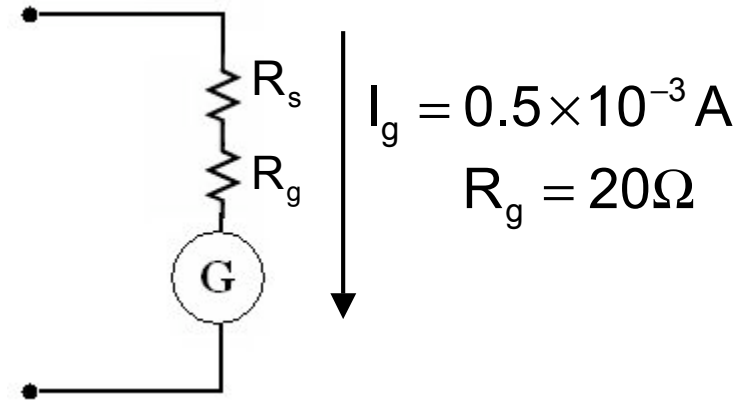

What is the value of R<sub>s</sub> now?

We need

$$10V = I_g(R_s + R_g)$$
$$R_s + R_g = \frac{10V}{I_g} = \frac{10V}{5 \times 10^{-4} A}$$
$$R_s + R_g = 20,000\Omega$$
$$R_s = 19,980\Omega$$

So, the shunt resistor needs to be about 20KΩ.

Note: the voltmeter is in parallel with the battery.