

5. (a) Let  $i$  be the current in the circuit and take it to be positive if it is to the left in  $R_1$ . We use Kirchhoff's loop rule:  $\mathcal{E}_1 - iR_2 - iR_1 - \mathcal{E}_2 = 0$ . We solve for  $i$ :

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{12 \text{ V} - 6.0 \text{ V}}{4.0 \Omega + 8.0 \Omega} = 0.50 \text{ A}.$$

A positive value is obtained, so the current is counterclockwise around the circuit.

If  $i$  is the current in a resistor  $R$ , then the power dissipated by that resistor is given by  $P = i^2 R$ .

(b) For  $R_1$ ,  $P_1 = (0.50 \text{ A})^2 (4.0 \Omega) = 1.0 \text{ W}$ ,

(c) and for  $R_2$ ,  $P_2 = (0.50 \text{ A})^2 (8.0 \Omega) = 2.0 \text{ W}$ .

If  $i$  is the current in a battery with emf  $\mathcal{E}$ , then the battery supplies energy at the rate  $P = i\mathcal{E}$  provided the current and emf are in the same direction. The battery absorbs energy at the rate  $P = i\mathcal{E}$  if the current and emf are in opposite directions.

(d) For  $\mathcal{E}_1$ ,  $P_1 = (0.50 \text{ A})(12 \text{ V}) = 6.0 \text{ W}$

(e) and for  $\mathcal{E}_2$ ,  $P_2 = (0.50 \text{ A})(6.0 \text{ V}) = 3.0 \text{ W}$ .

(f) In battery 1 the current is in the same direction as the emf. Therefore, this battery supplies energy to the circuit; the battery is discharging.

(g) The current in battery 2 is opposite the direction of the emf, so this battery absorbs energy from the circuit. It is charging.