

74. (a) If  $S_1$  is closed, and  $S_2$  and  $S_3$  are open, then  $i_a = \mathcal{E}/2R_1 = 120 \text{ V}/40.0 \text{ } \Omega = 3.00 \text{ A}$ .

(b) If  $S_3$  is open while  $S_1$  and  $S_2$  remain closed, then

$$R_{\text{eq}} = R_1 + R_1 (R_1 + R_2) / (2R_1 + R_2) = 20.0 \text{ } \Omega + (20.0 \text{ } \Omega) \times (30.0 \text{ } \Omega) / (50.0 \text{ } \Omega) = 32.0 \text{ } \Omega,$$

so  $i_a = \mathcal{E}/R_{\text{eq}} = 120 \text{ V}/32.0 \text{ } \Omega = 3.75 \text{ A}$ .

(c) If all three switches  $S_1$ ,  $S_2$  and  $S_3$  are closed, then  $R_{\text{eq}} = R_1 + R_1 R' / (R_1 + R')$  where

$$R' = R_2 + R_1 (R_1 + R_2) / (2R_1 + R_2) = 22.0 \text{ } \Omega,$$

i.e.,

$$R_{\text{eq}} = 20.0 \text{ } \Omega + (20.0 \text{ } \Omega) (22.0 \text{ } \Omega) / (20.0 \text{ } \Omega + 22.0 \text{ } \Omega) = 30.5 \text{ } \Omega,$$

so  $i_a = \mathcal{E}/R_{\text{eq}} = 120 \text{ V}/30.5 \text{ } \Omega = 3.94 \text{ A}$ .